



COMSM1302

Overview of Computer Architecture

Lecture 8

Simple CPU



The next step.

Transistors

- PMOS
- NMOS

Logic gates

- NOT
- NAND
- NOR

Simple devices

- Ripple-carry adder-subtractor
- Mux and demux

Memory

- Registers from D-type flip flops
- SRAM
- DRAM

CPU

- Registers
- ALU
- Memory
- CU



What we will learn in Part 2


1. Week 5 and 7: Central Processing Unit (CPU) architecture
2. Week 8 and 9: ARM instruction set architecture and assembly programming.
3. Week 10: Assemblers and Compilers.





In this lecture

 
1. Computer layers from hardware to software.
2. From 4-bit counter to 4-bit CPU



- Review memory, data sizes and clock
- Small assembly program




Layers

 




 From 4-bit counter to 4-bit CPU - Counter




4-bit counter

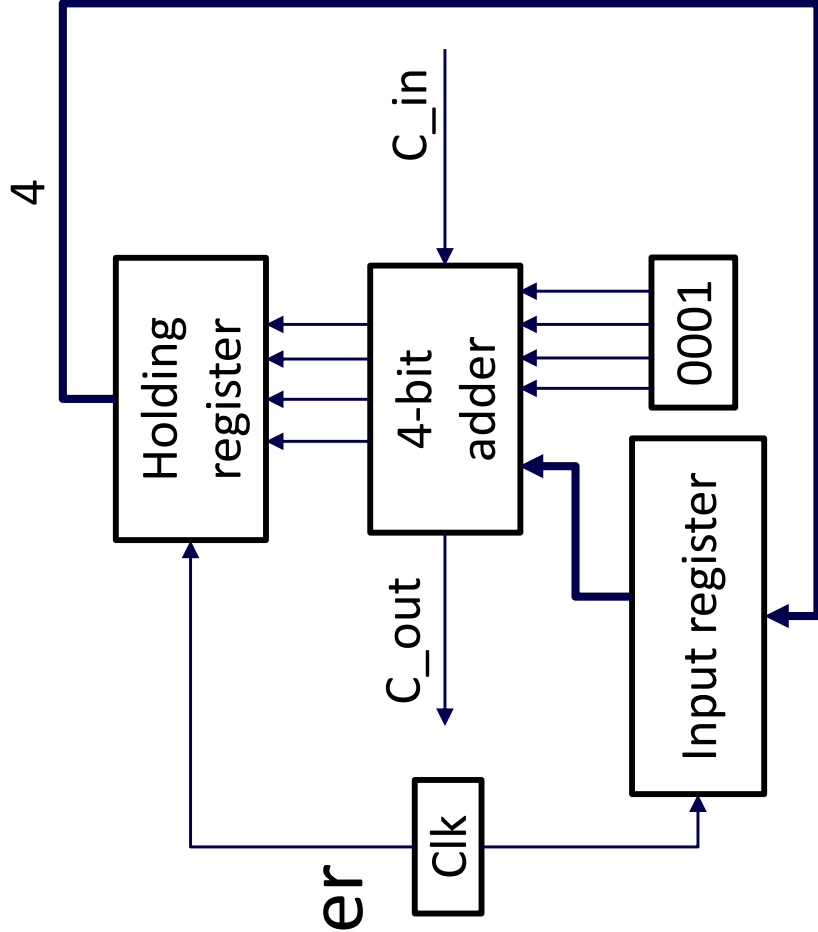- Design a 4-bit counter:
 - 4-bit adder
 - Constant one
 - High level triggered register
 - Holding register
 - Input register
 - Clock




4-bit counter - questions

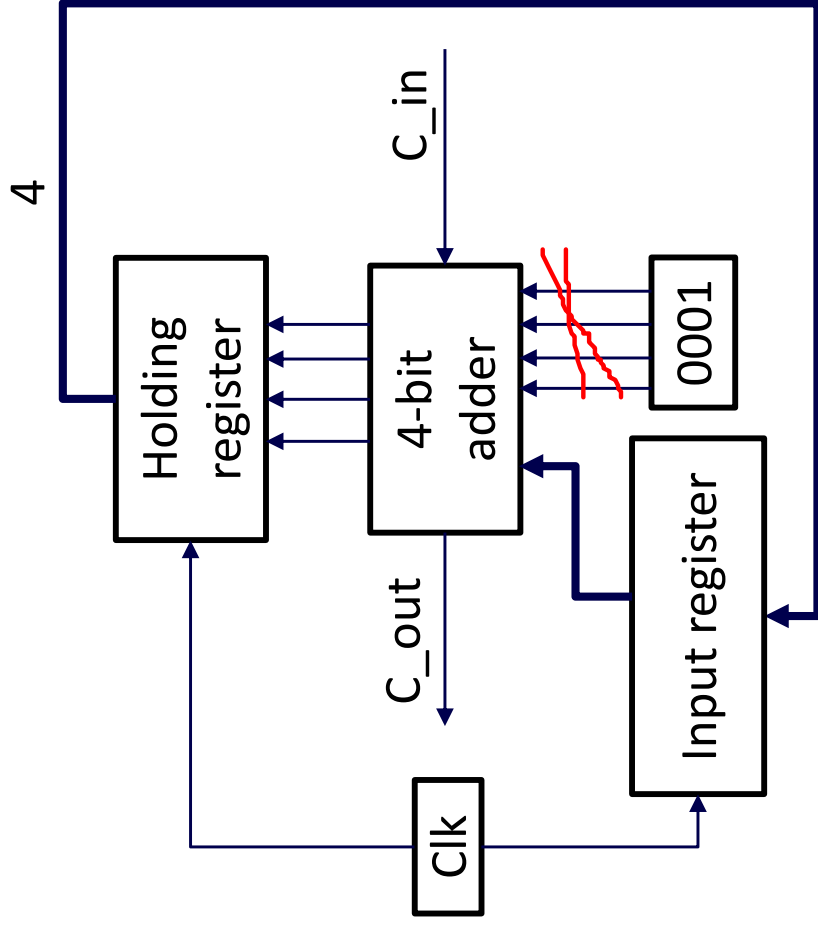1. What is the range of this counter with and without considering the carry out bit?
2. Can you leave the second input disconnected and still achieve the same functionality? What should we use instead?






4-bit counter – (1/5)

 

| CLK | Reg A | Adder | H Reg |
|-----|-------|-------|-------|
| 1a | 0000 | 0001 | 0001 |
| 1b | | | |
| 2a | | | |
| 2b | | | |
| 3a | | | |
| 3b | | | |

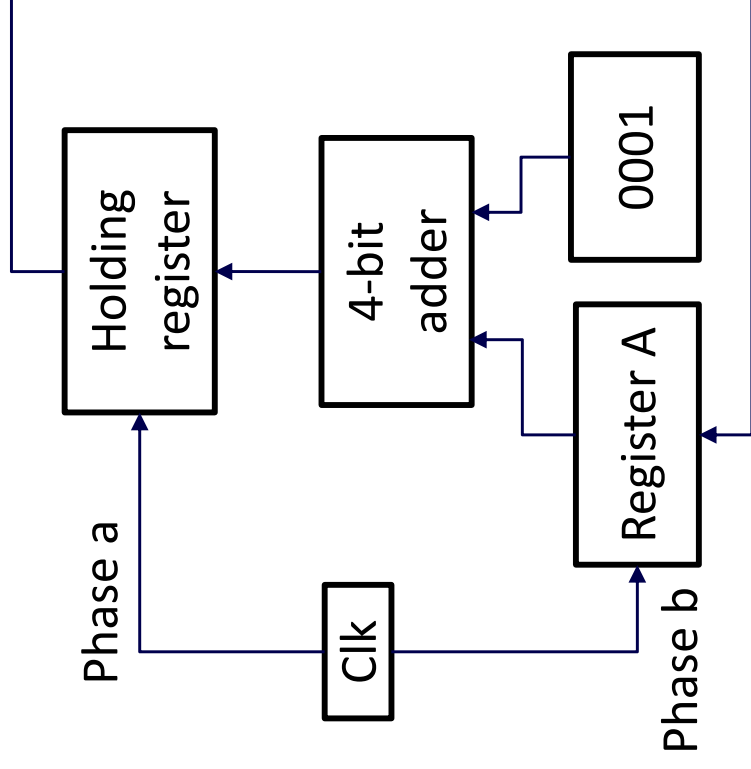


Assume A initial value is 0000






4-bit counter – (2/5)

 

| CLK | Reg A | Adder | H Reg |
|-----|-------|-------|-------|
| 1a | 0000 | 0001 | 0001 |
| 1b | 0001 | 0010 | 0001 |
| 2a | | | |
| 2b | | | |
| 3a | | | |
| 3b | | | |

 


Assume A initial value is 0000






4-bit counter – (3/5)

 

| CLK | Reg A | Adder | H Reg |
|-----|-------|-------|-------|
| 1a | 0000 | 0001 | 0001 |
| 1b | 0001 | 0010 | 0001 |
| 2a | 0001 | 0010 | 0010 |
| 2b | | | |
| 3a | | | |
| 3b | | | |


 


Assume A initial value is 0000





4-bit counter – (4/5)

  



Assume A initial value is 0000

| CLK | Reg A | Adder | H Reg |
|-----|-------|-------|-------|
| 1a | 0000 | 0001 | 0001 |
| 1b | 0001 | 0010 | 0001 |
| 2a | 0001 | 0010 | 0010 |
| 2b | 0010 | 0011 | 0010 |
| 3a | | | |
| 3b | | | |





4-bit counter – (5/5)

  


Assume A initial value is 0000


| CLK | Reg A | Adder | H Reg |
|-----|-------|-------|-------|
| 1a | 0000 | 0001 | 0001 |
| 1b | 0001 | 0010 | 0001 |
| 2a | 0001 | 0010 | 0010 |
| 2b | 0010 | 0011 | 0010 |
| 3a | | | |
| 3b | | | |



4-bit counter – example - 2

 

| CLK | Reg A | Adder | H Reg |
|-----|-------|-------|-------|
| 1a | 1101 | 1110 | 1110 |
| 1b | | | |
| 2a | | | |
| 2b | | | |
| 3a | | | |
| 3b | | | |

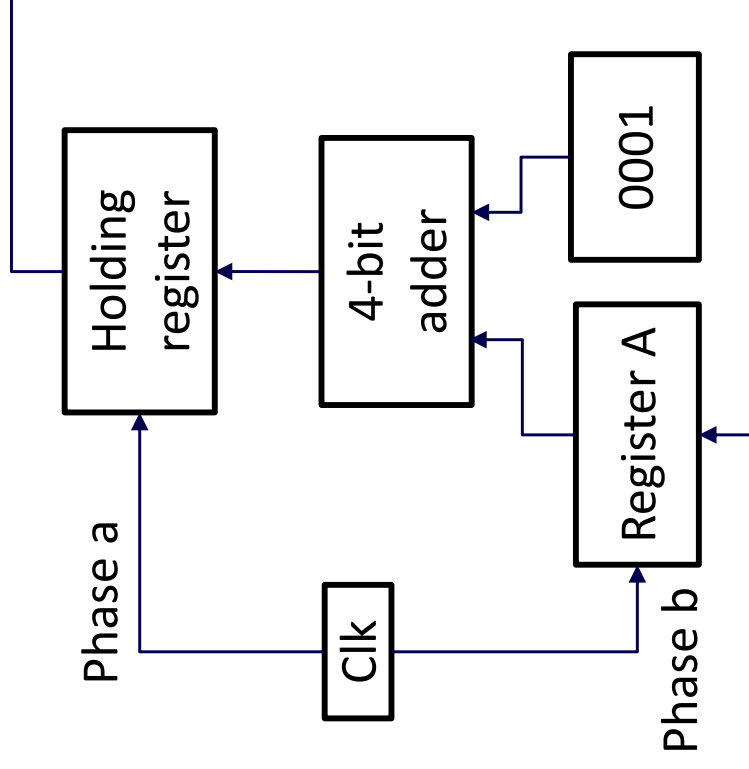



Assume A initial value is 1101








4-BIT BINARY FULL ADDDER

U

 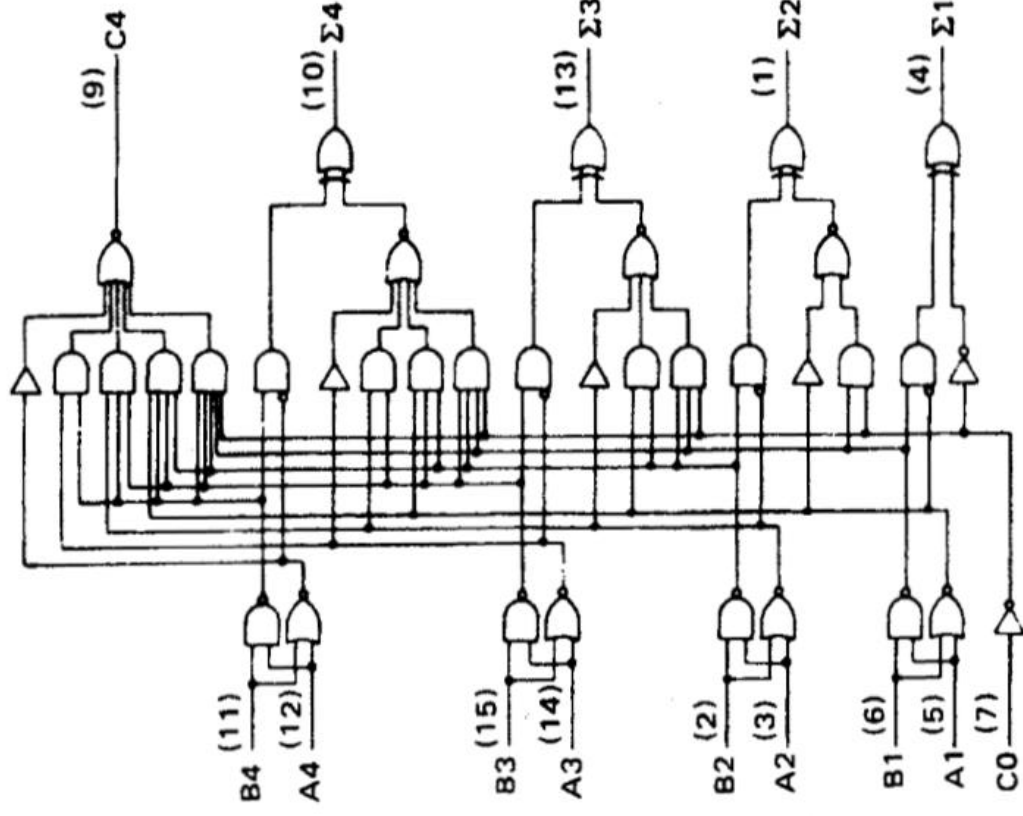


Registers

   




 From 4-bit counter to 4-bit CPU - Accumulator



Accumulator

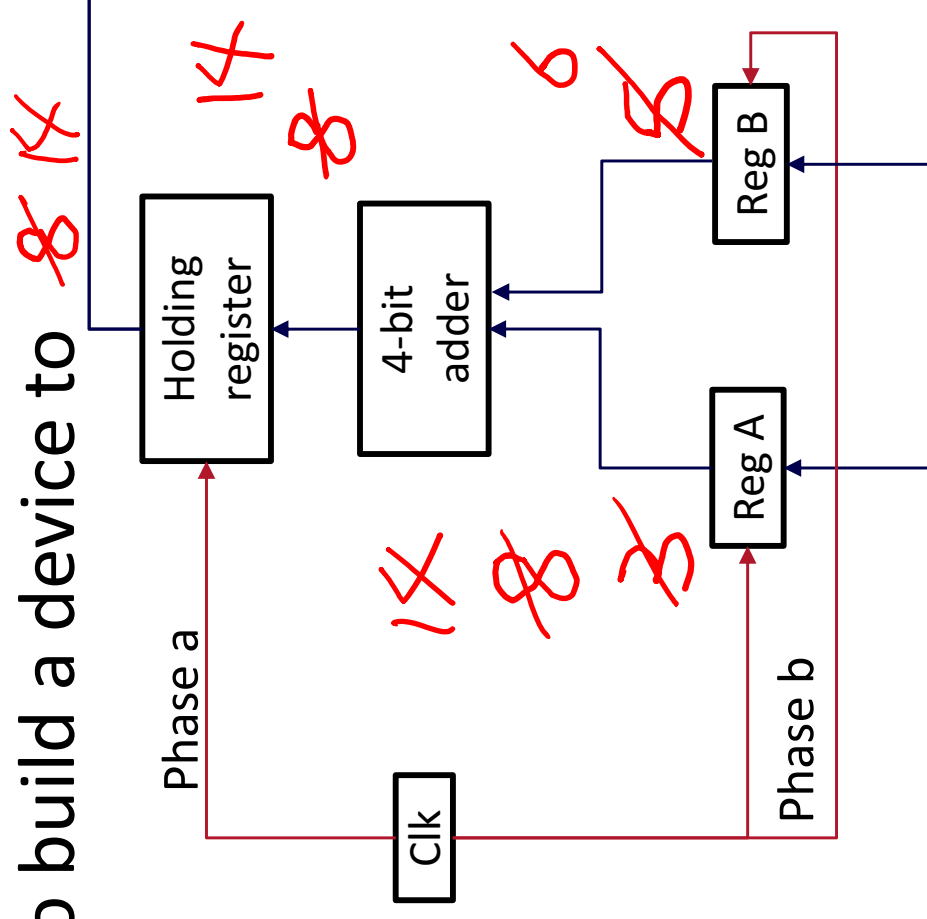- Upgrade our 4-bit counter to build a device to ~~8~~ ¹⁴
- accumulate numbers.
- How to sum 3, 5, and 6.
 1. Start from cleared registers
 2. Load 3 to A
 3. Load 5 to B
 4. Store sum of A and B in A 8
 5. Load 6 to B
 6. Store sum of A and B in A 14





Simple data path – thinking questions




- Think about
 1. How to load the input numbers to the registers?
 2. How will we control which register A or B to update when they are both connected to the same clock phase?
 3. How to switch between the input device and registers?



Simple data path – advanced design

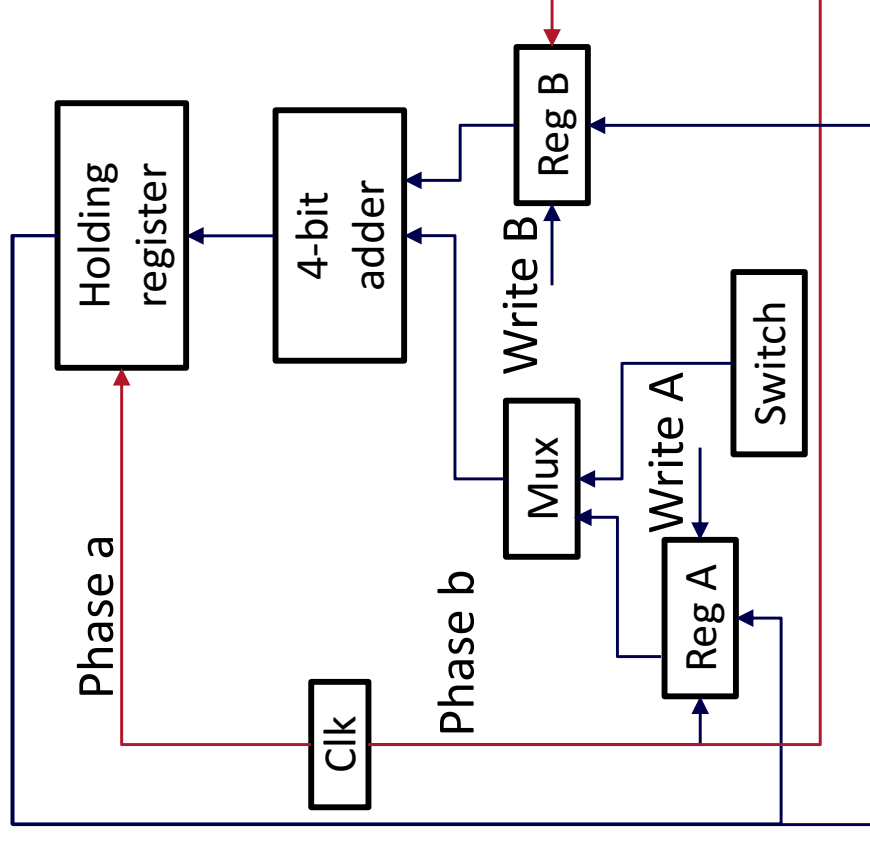1. To input number, we need a 4-bit switch.
2. To control which registers to write to in the clock phase b, we need a control signal (1: enable, 0: disable).
3. To choose between the input-switch and the register A, we need a mux.






Simple data path (1/5)



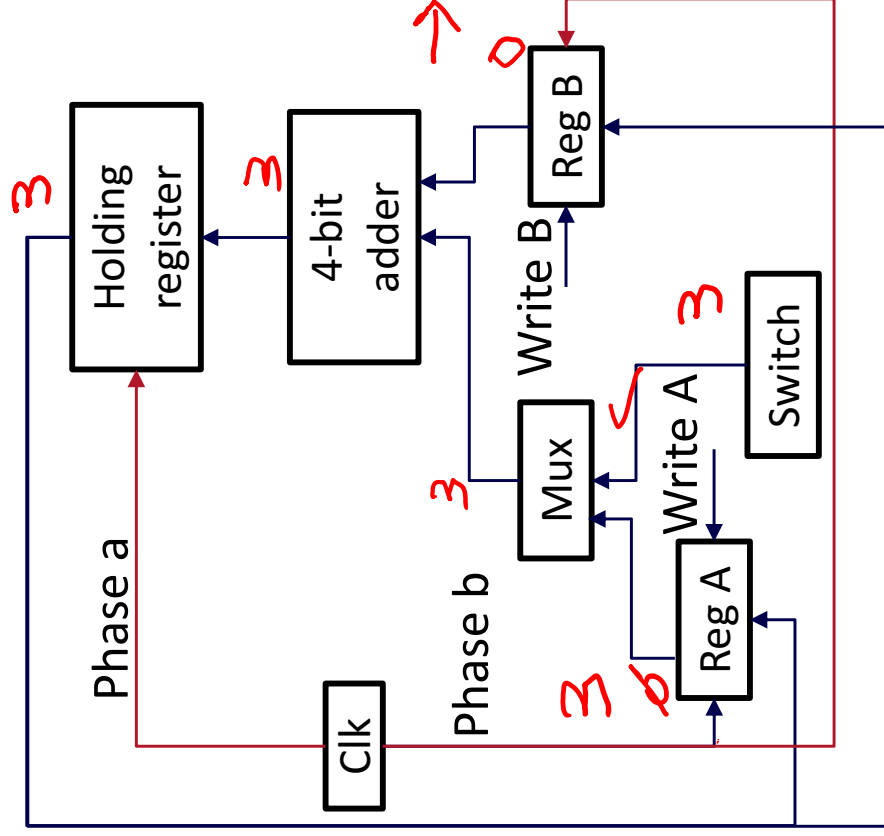- Add 3,5, and 6 and store the result in register A.




| Clk | SW | Mux | Write A | Write B | A | B | Adder |
|-----|------|-----|---------|---------|------|------|-------|
| 1a | 0011 | SW | x | x | 0000 | 0000 | |
| 1b | 0011 | SW | True | False | 0011 | 0000 | |
| 2a | | | | | | | |
| 2b | | | | | | | |
| 3a | | | | | | | |
| 3b | | | | | | | |





Simple data path (2/5)

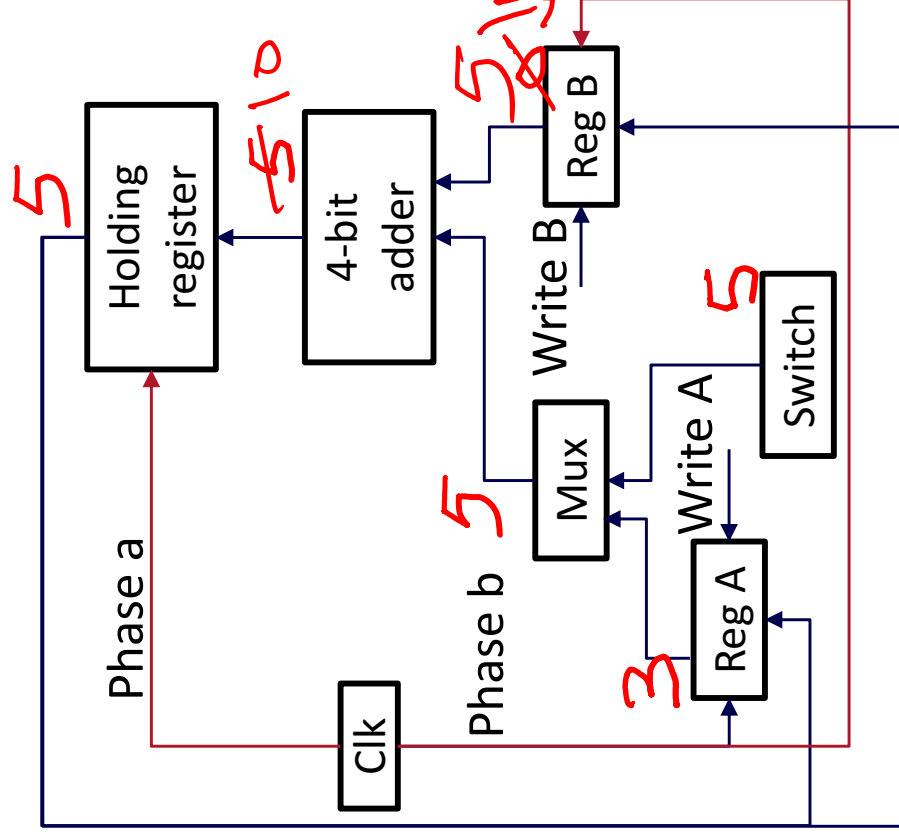

- Add 3, 5, and 6 and store the result in register A.


| Clk | SW | Mux | Write A | Write B | A | B | Adder |
|-----|------|-----|---------|---------|------|------|-------|
| 1a | 0011 | SW | x | x | 0000 | 0000 | 0011 |
| 1b | 0011 | SW | True | False | 0011 | 0000 | 0011 |
| 2a | 0101 | SW | x | x | 0011 | 0000 | 0101 |
| 2b | 0101 | SW | False | True | 0011 | 0101 | 1010 |
| 3a | | | | | | | |
| 3b | | | | | | | |





Simple data path (3/5)

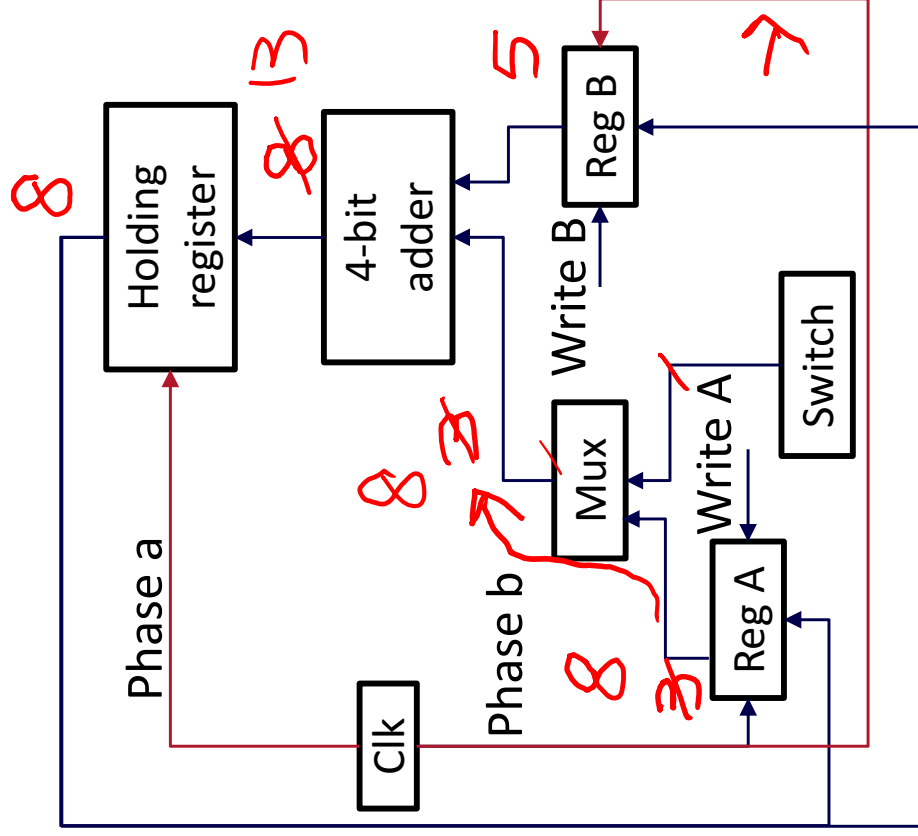- Add 3,5, and 6 and store the result in register A.




| Clk | SW | Mux | Write A | Write B | A | B | Adder |
|-----|------|-------|---------|---------|------|------|-------|
| 1a | 0011 | SW | x | x | 0000 | 0000 | 0011 |
| 1b | 0011 | SW | True | False | 0011 | 0000 | 0011 |
| 2a | 0101 | SW | x | x | 0011 | 0000 | 0101 |
| 2b | 0101 | SW | False | True | 0011 | 0101 | 1010 |
| 3a | x | Reg A | x | x | 0011 | 0101 | 1000 |
| 3b | x | Reg A | True | False | 1000 | 0101 | 1101 |





Simple data path (4/5)

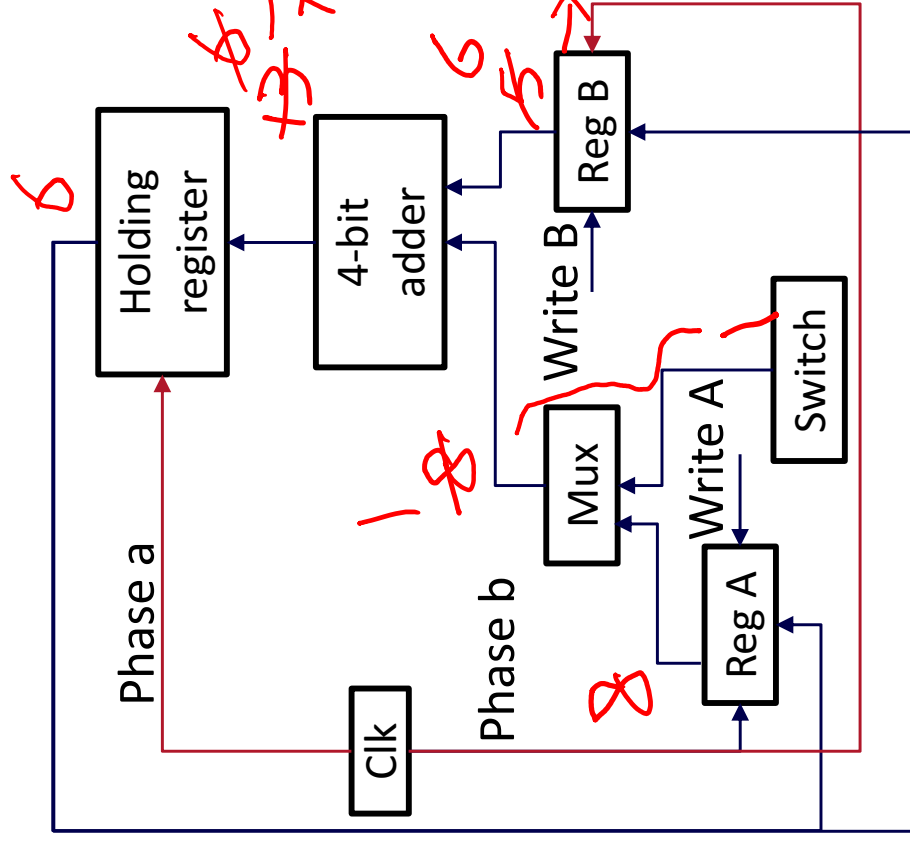
- Add 3, 5, and 6 and store the result in register A.





Simple data path (5/5)

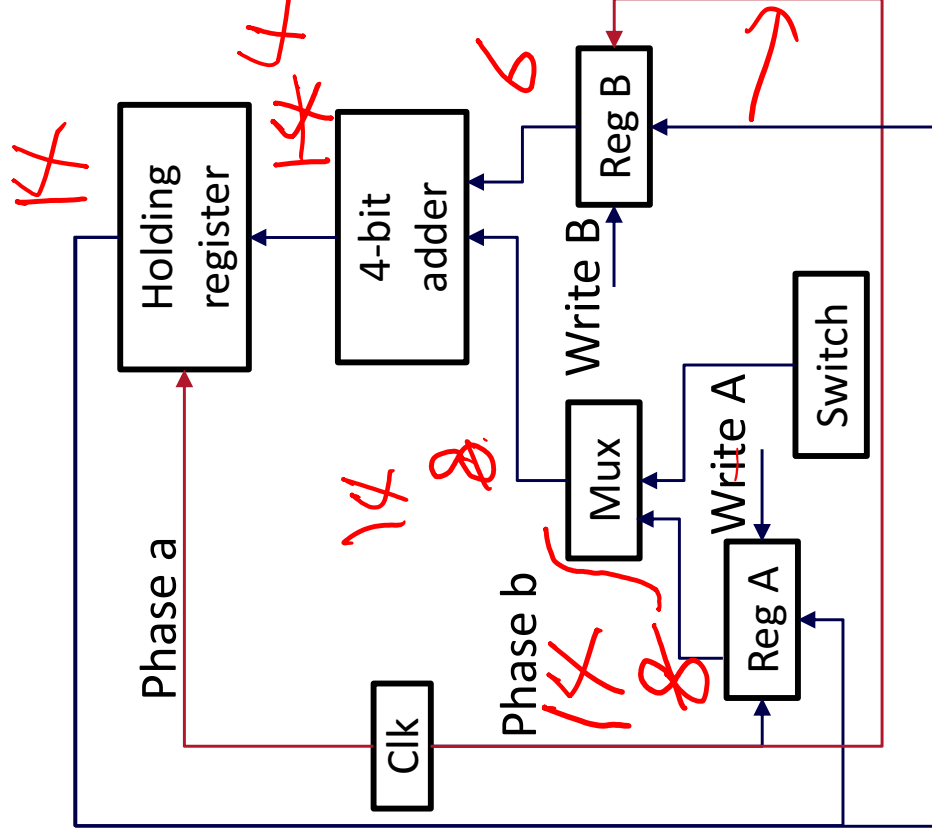- Add 3,5, and 6 and store the result in register A.




| Clk | SW | Mux | Write A | Write B | A | B | Adder |
|-----|------|-------|---------|---------|------|------|-------|
| 3a | x | Reg A | x | x | 0011 | 0101 | 1000 |
| 3b | x | Reg A | True | False | 1000 | 0101 | 1101 |
| 4a | 0001 | SW | x | x | 1000 | 0101 | 0110 |
| 4b | 0001 | SW | False | True | 1000 | 0110 | 0111 |
| 5a | x | Reg A | x | x | 1000 | 0110 | 1110 |
| 5b | x | Reg A | True | False | 1110 | 0110 | 0100 |





From 4-bit counter to 4-bit CPU

– Data path

 






From 4-bit counter to 4-bit CPU

– Data path

 



4-bit CPU concept



1. Store data and instructions in memory.
2. Fetch instruction from memory.
3. Execute these instructions.





Data in memory

- How are data stored in memory?

- Data sizes:

- Nibble = 4 bits
- Byte = 8 bits
- Halfword = 16 bits
- Word = 32 bits

- Store 3, 5, and 6.

Data


| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | Address |
|-----|-----|-----|-----|-----|-----|-----|-----|---------|
| x | x | x | x | 0 | 0 | 1 | 1 | 0b0000 |
| x | x | x | x | 0 | 1 | 0 | 1 | 0b0001 |
| x | x | x | x | 0 | 1 | 1 | 0 | 0b0010 |
| x | x | x | x | x | x | x | x | 0b0011 |
| ... | ... | ... | ... | ... | ... | ... | ... | ... |
| x | x | x | x | x | x | x | x | 0b1111 |





Instructions in memory

- Add 3,5, and 6, then subtract 2

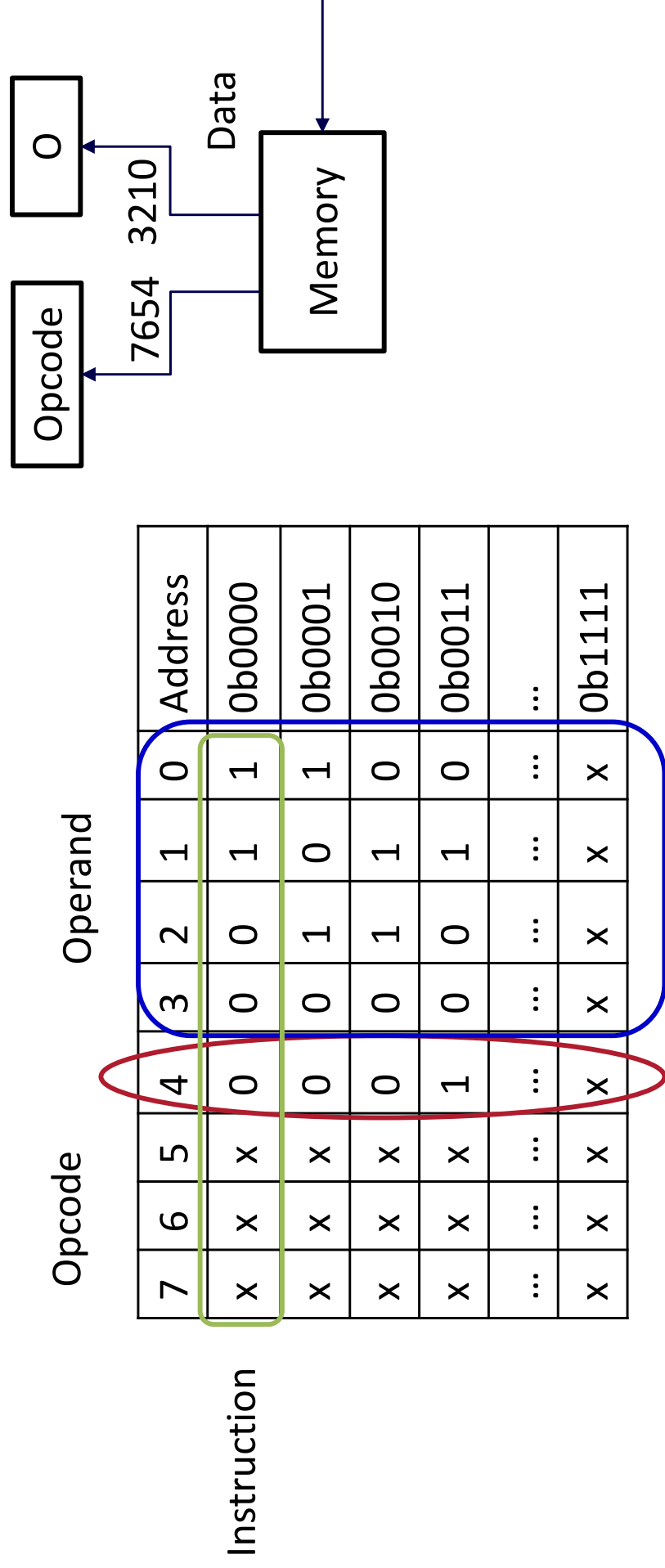



4-bit CPU concept




1. Store data and instructions in memory.
2. Fetch instruction from memory.
3. Execute these instructions.





Fetch instructions (1/4)


- Add 3,5, and 6, then subtract 2

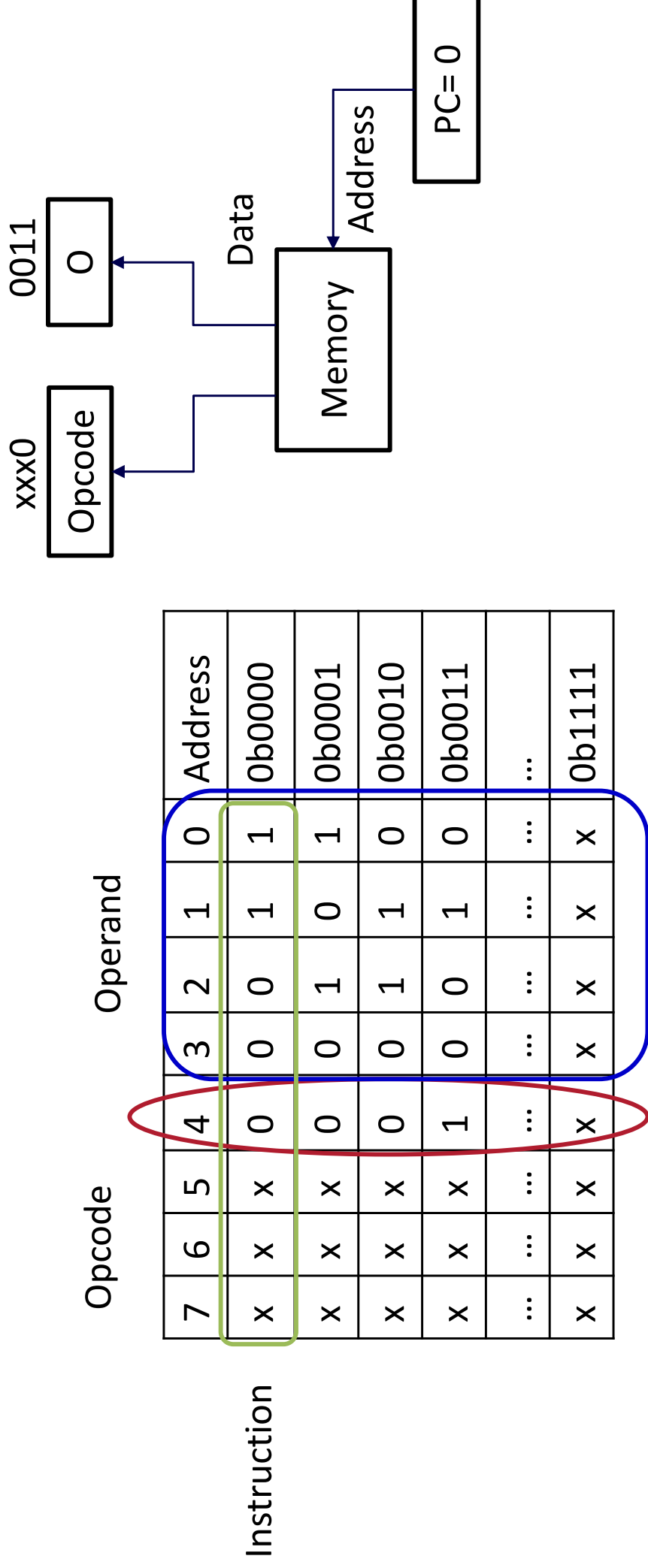



Fetch instructions (2/4)


- Add 3,5, and 6, then subtract 2

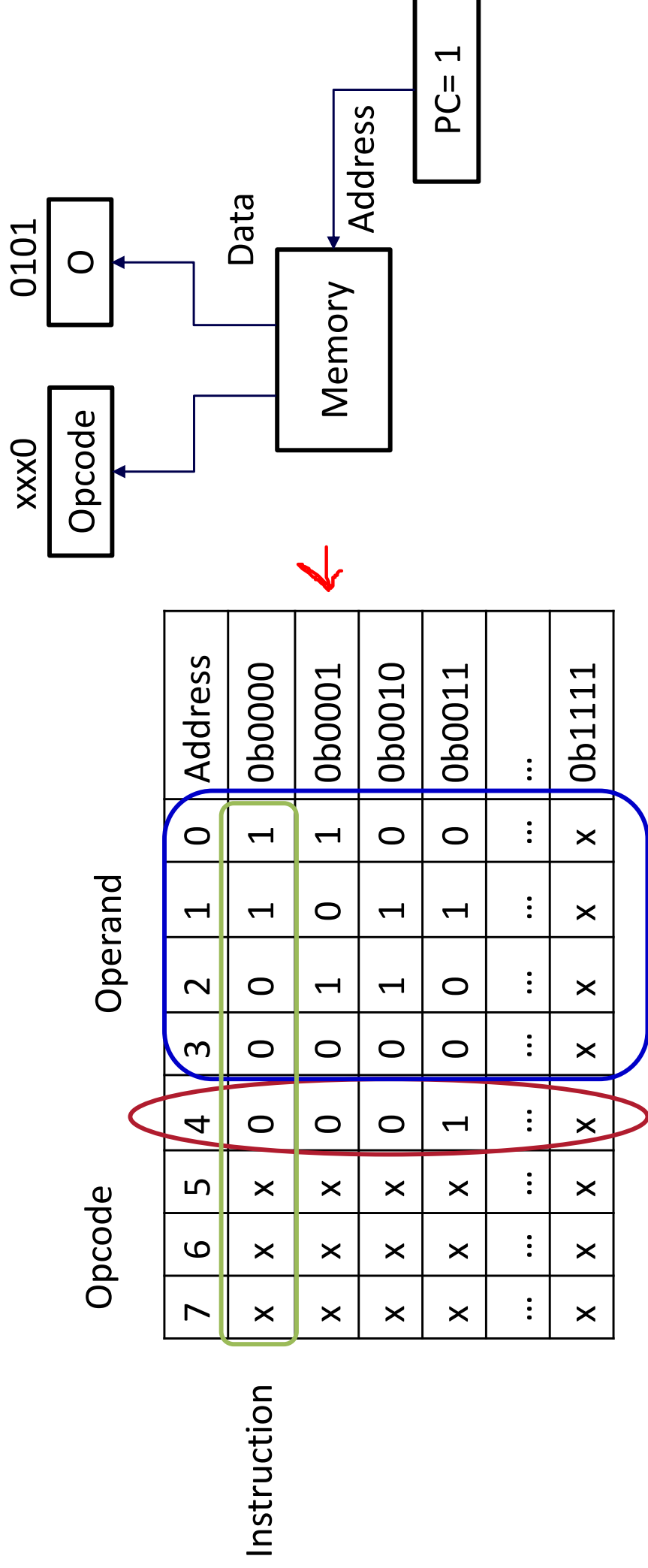



Fetch instructions (3/4)

- Add 3,5, and 6, then subtract 2

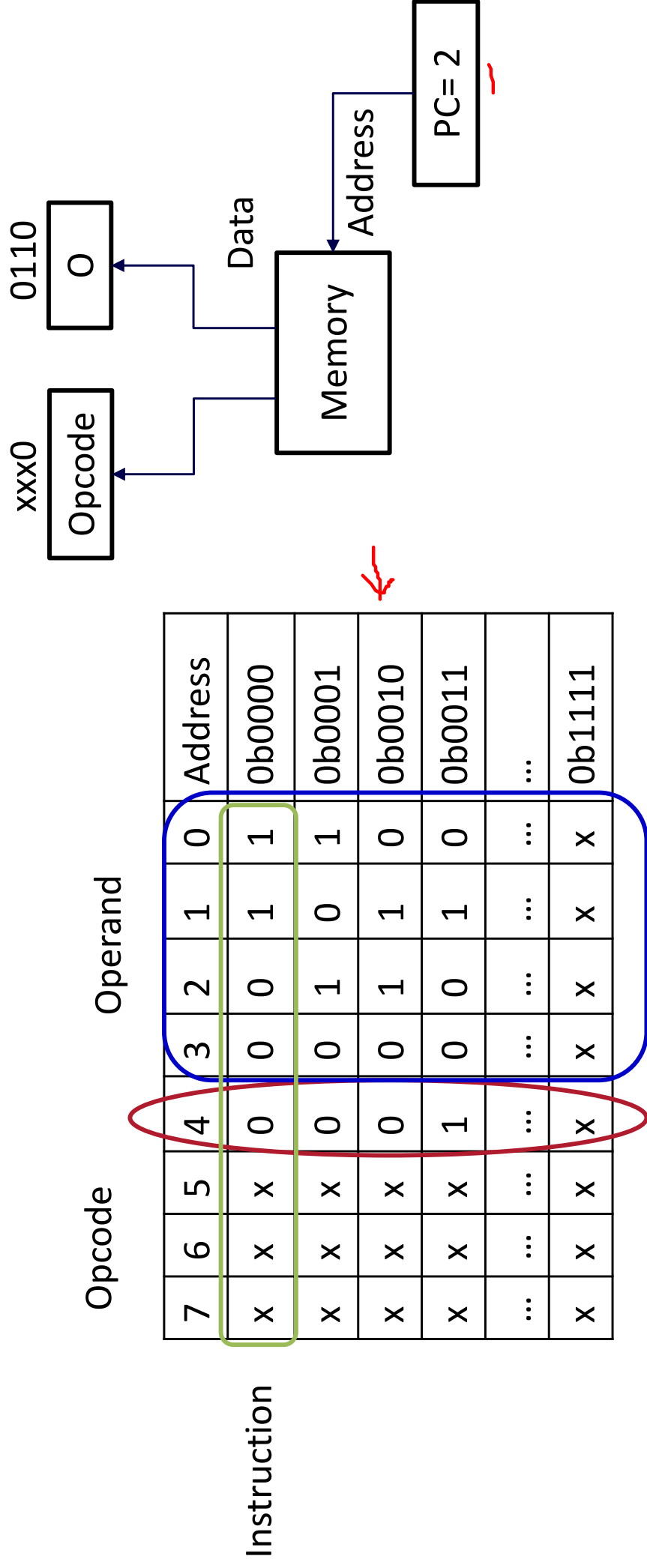




Fetch instructions (4/4)


- Add 3, 5, and 6, then subtract 2¹

$A = \sqrt{2}$

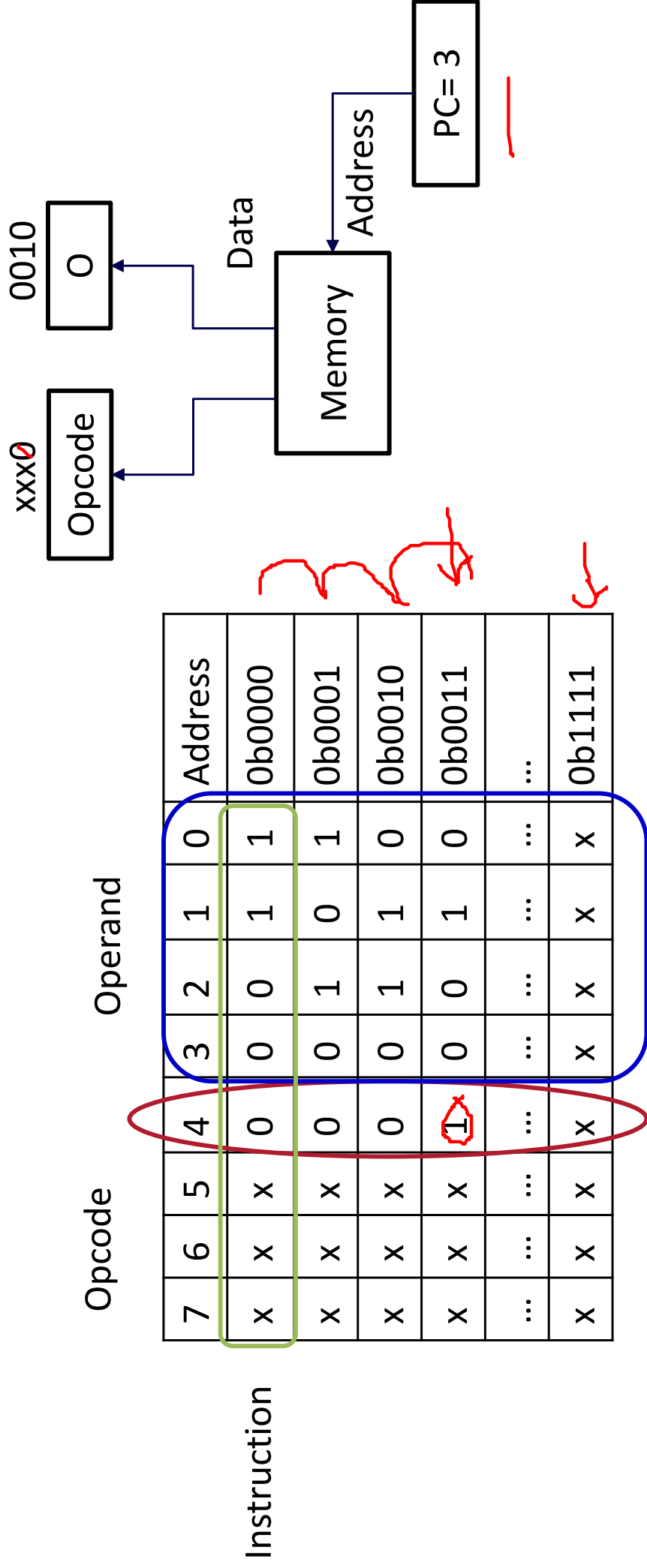



Program counter

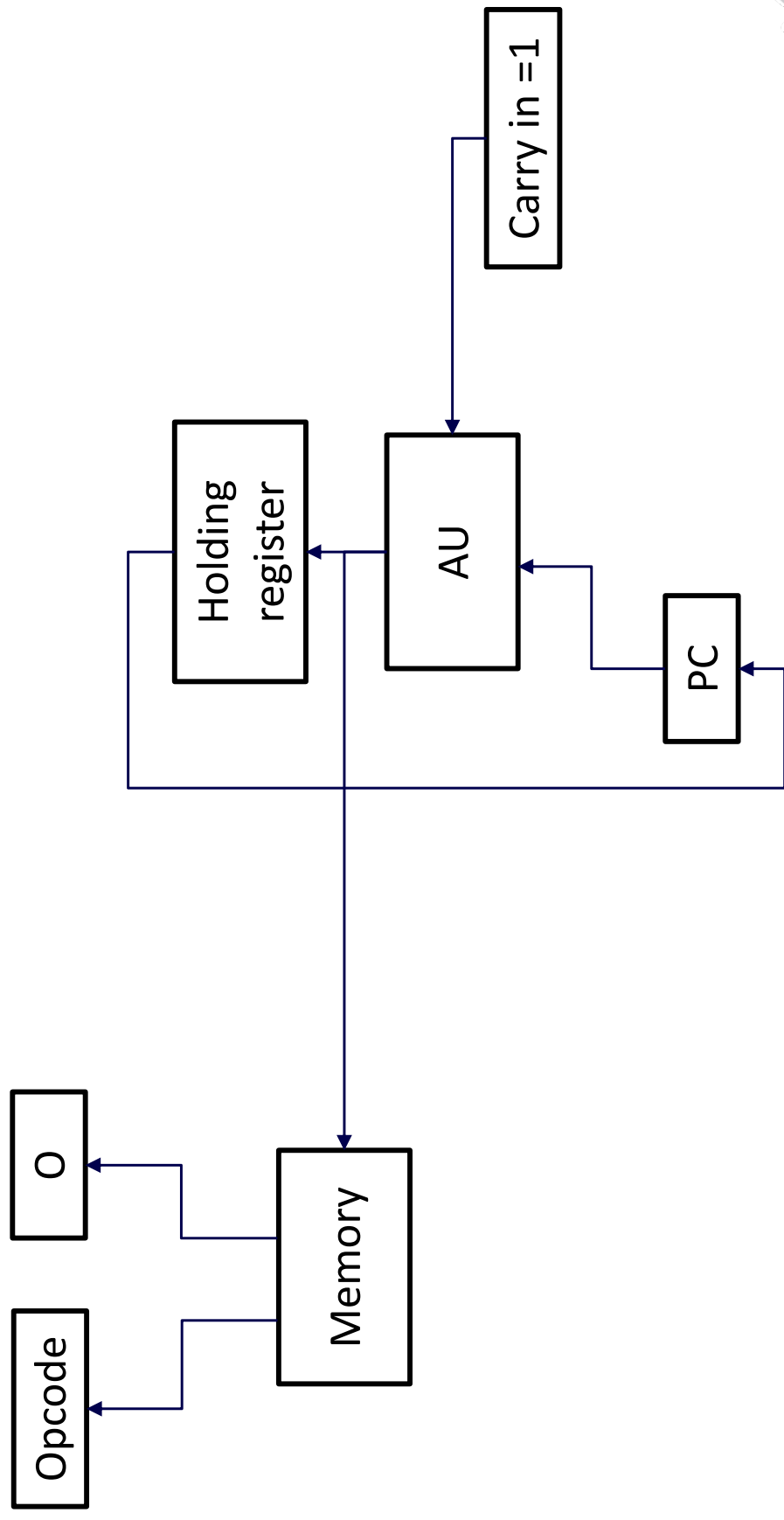






4-bit CPU concept



1. Store data and instructions in memory.
2. Fetch instruction from memory.
3. Execute these instructions.





4-bit CPU

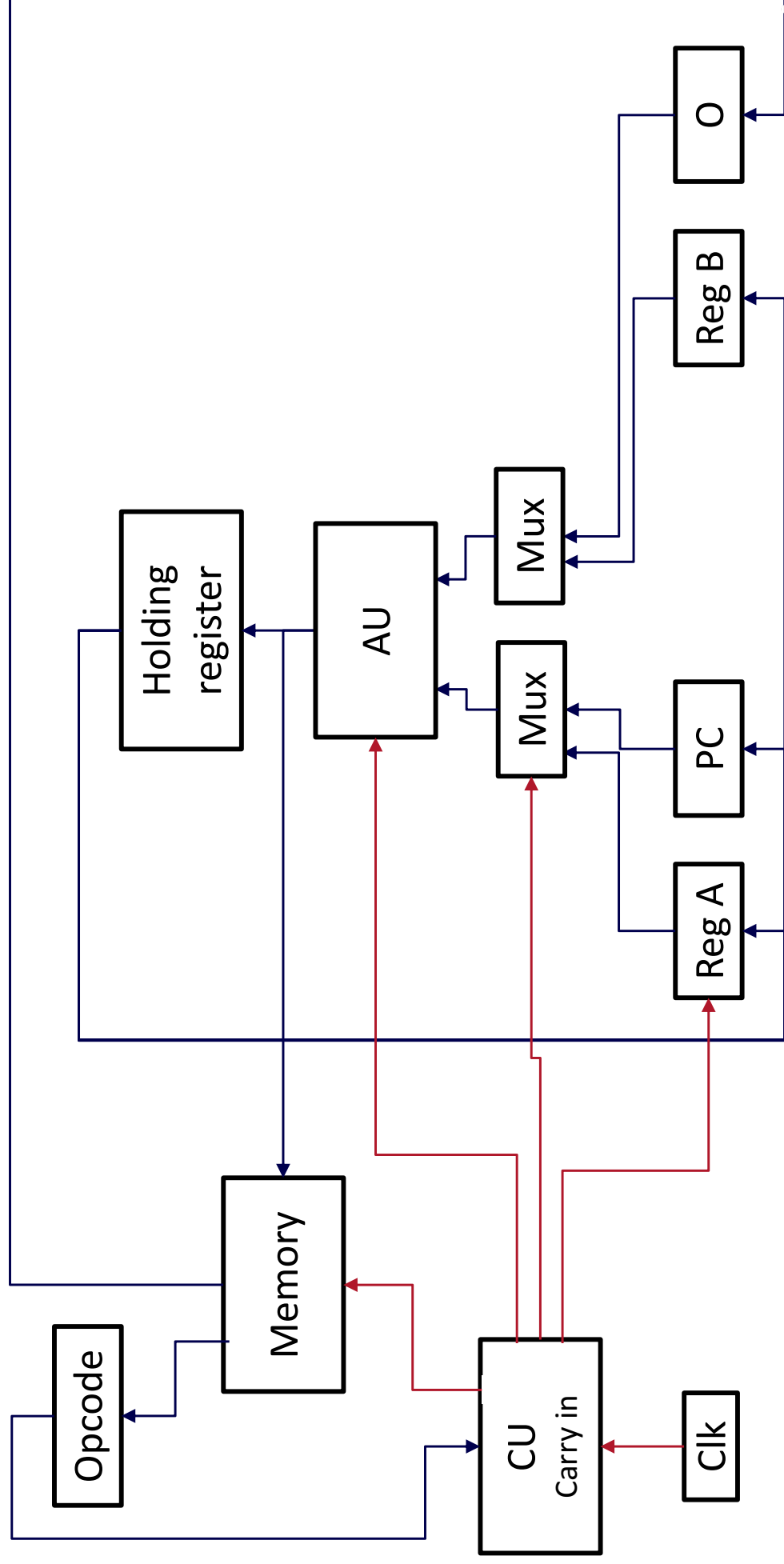



Summary

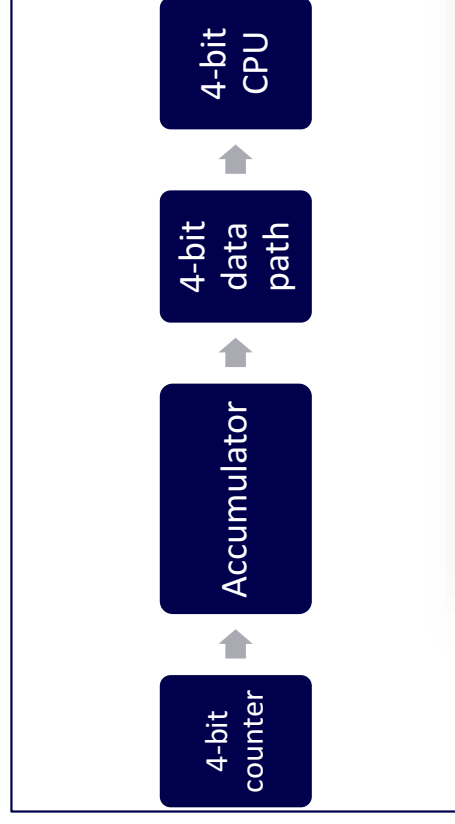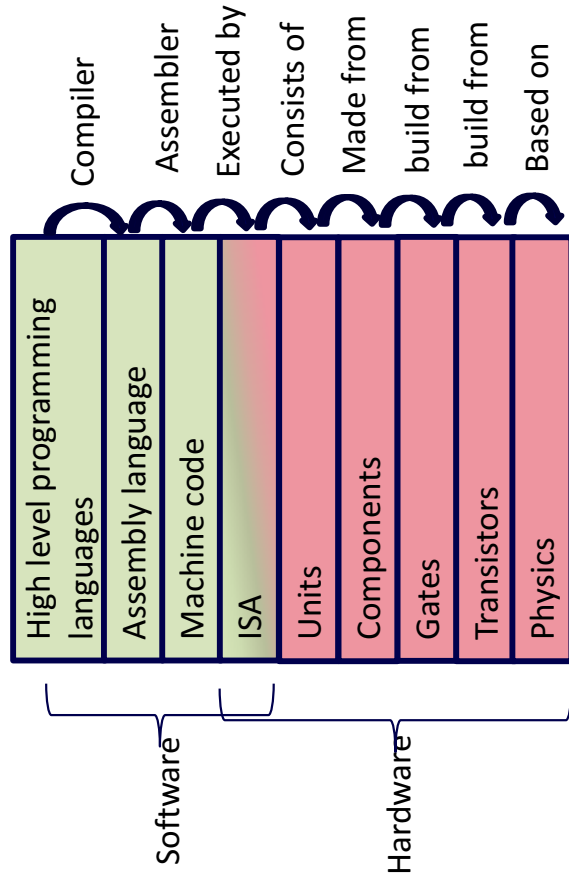

| Opcode | | | | Operand | | | | Address |
|--------|-----|-----|-----|---------|-----|-----|-----|---------|
| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | |
| x | x | x | 0 | 0 | 0 | 1 | 1 | 0b0000 |
| x | x | x | 0 | 0 | 1 | 0 | 1 | 0b0001 |
| x | x | x | 0 | 0 | 1 | 1 | 0 | 0b0010 |
| x | x | x | 1 | 0 | 0 | 1 | 0 | 0b0011 |
| ... | ... | ... | ... | ... | ... | ... | ... | ... |
| x | x | x | x | x | x | x | x | 0b1111 |

How to sum 3, 5, and 6.

1. Start from cleared registers
2. Load 3 to A
3. Load 5 to B
4. Store sum of A and B in A
5. Load 6 to B
6. Store sum of A and B in A

