

# COMSM1302

## Overview of Computer Architecture

### Lecture 3

### Transistor logic and CMOS



# In this lecture

## Foundations

- Data representation, logic, Boolean algebra.

## Building blocks

- **Transistors, transistor based logic**, simple devices, storage.

## Modules

- Memory, simple controllers, FSMs, processors and execution.

## Programming

- Machine code, assembly, high-level languages, compilers.



## Wrap-up

- Operating systems, energy aware computing.



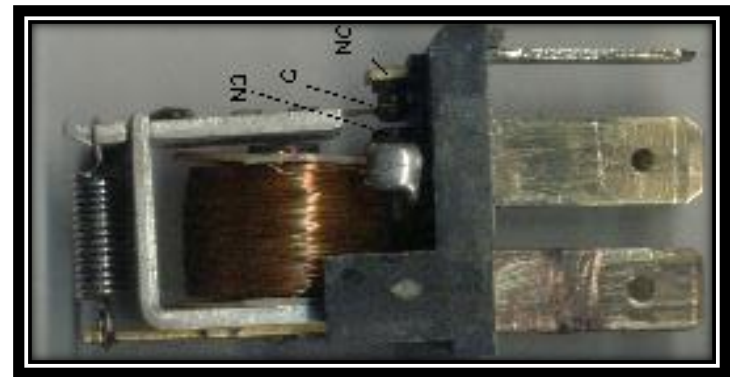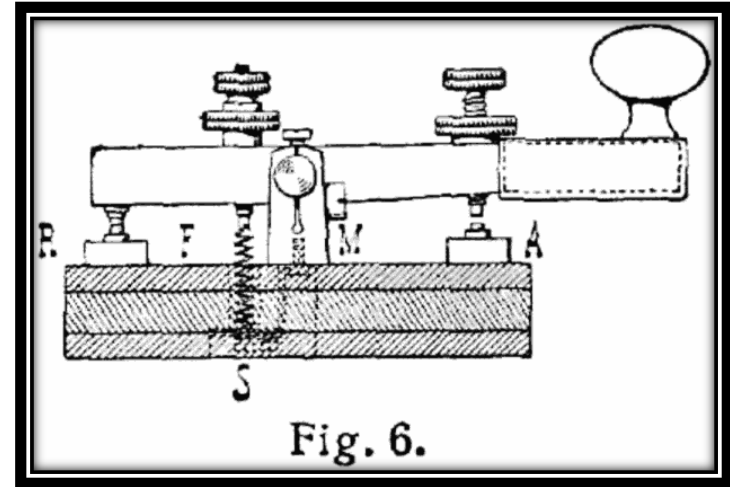
# 🔥 The switch - mechanical

- Mechanical switches are very useful
  - Turn things on/off
  - With several switches, we can **encode** more useful things.
- What's wrong with them?



# 🔥 The switch - valve

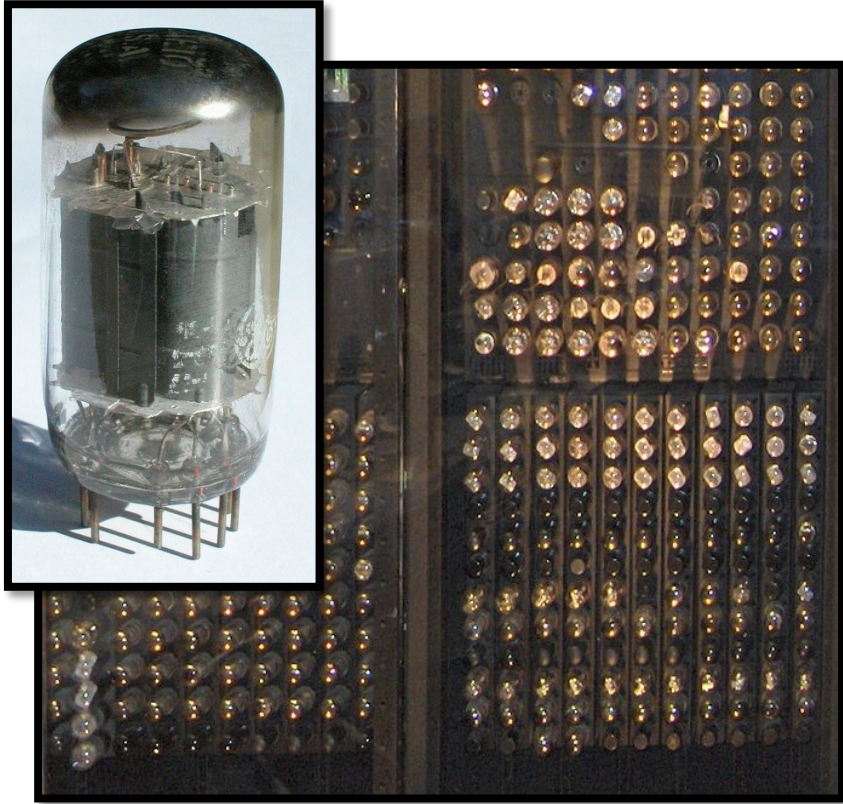

Bank of valves from the ENIAC computer (1946).

Photo [source](#): TexDex, Wikimedia Commons.

- Valves or vacuum tubes.
- Current controlled by **thermionic emission**.
  - They have a **heating element**.
- Quicker than mechanical switches.
- Fairly reliable
  - **If they're kept on!**
  - *ENIAC (1946) used 17,468 vacuum tubes and consumed 150 kW of power.*



# The switch - silicon

- Silicon, the element “Si”
  - The second most **abundant element** on Earth.
- A **semiconductor**
  - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.



# 🔥 The switch – silicon old

- Silicon, the element “Si”
  - The second most **abundant element** on Earth.
- A **semiconductor**
  - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

🔥 Ore




🔥 Boule



[Source](#): Stahlkocher, Wikimedia Commons

🔥 Wafer

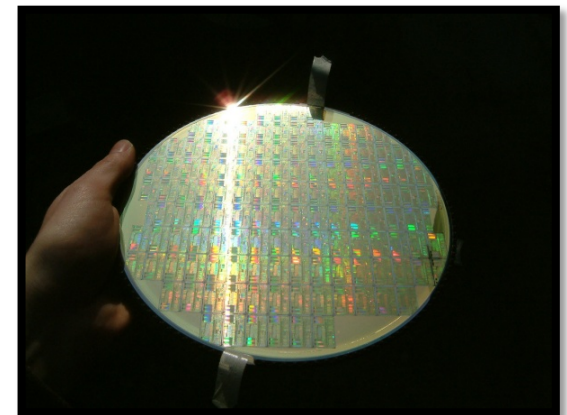

Source: James Irwin, [CC 2.0](#)





# The switch - silicon

- Silicon, the element “Si”
  - The second most **abundant element** on Earth.
- A **semiconductor**
  - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

## Ore



[Source](#): Stahlkocher, Wikimedia Commons



# 🔥 The switch - silicon

- Silicon, the element “Si”
  - The second most **abundant element** on Earth.
- A **semiconductor**
  - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

🔥 Ore



🔥 Boule



[Source](#): Stahlkocher, Wikimedia Commons





# 🔥 The switch - silicon

- Silicon, the element “Si”
  - The second most **abundant element** on Earth.
- A **semiconductor**
  - Can be constructed (using a process called **doping**) to pass electrons through a channel, when a voltage is applied to a **gate**.

🔥 Ore




🔥 Boule



[Source](#): Stahlkocher, Wikimedia Commons

🔥 Wafer

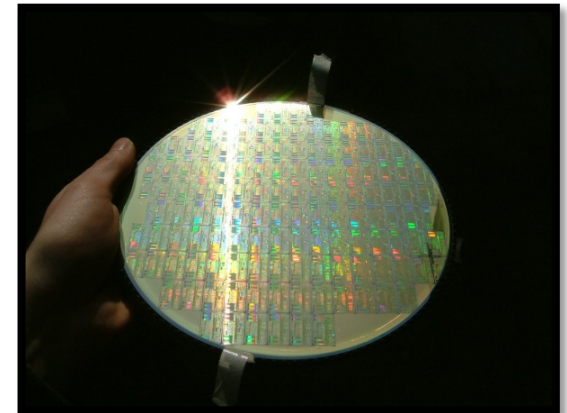


Source: James Irwin, [CC 2.0](#)



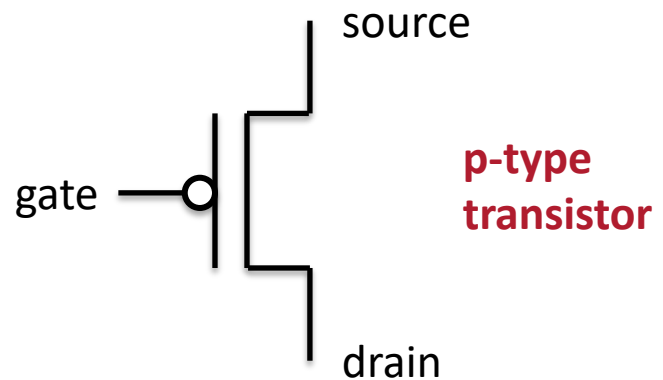
# 🔥 Making a switch out of silicon

- The **transistor**
  - Was invented in 1947 at AT&T's Bell Labs.
- Multiple uses
  - Amplification
  - **Switching**
- Multiple methods of construction
- We are interested in **Integrated Circuits** (ICs), so we want:  
**Complementary Metal–Oxide–Semiconductor (CMOS) technology.**



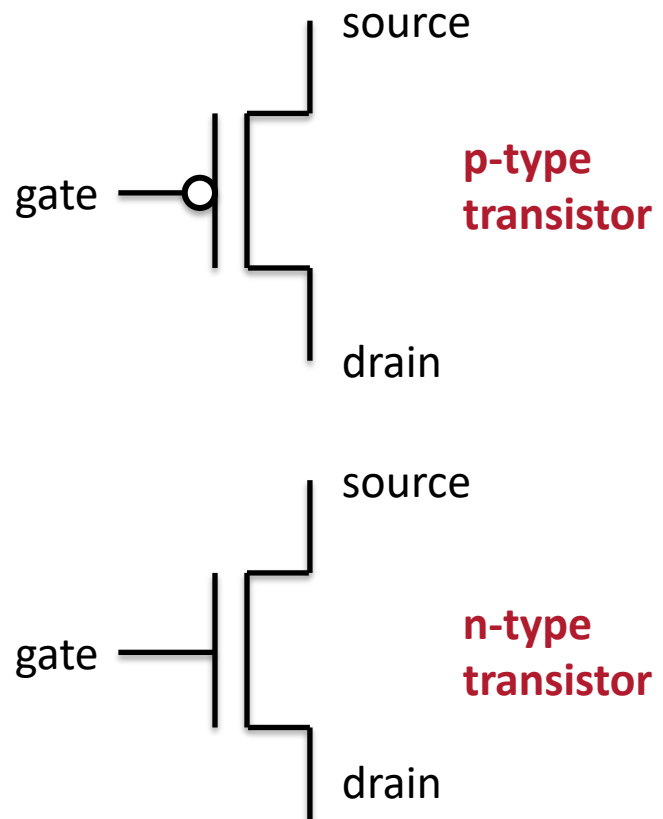
# 🔥 Making a switch out of silicon

- The **transistor**
  - Was invented in 1947 at AT&T's Bell Labs.
- Multiple uses
  - Amplification
  - **Switching**
- Multiple methods of construction
- We are interested in **Integrated Circuits** (ICs), so we want:  
**Complementary Metal–Oxide–Semiconductor (CMOS)** technology.


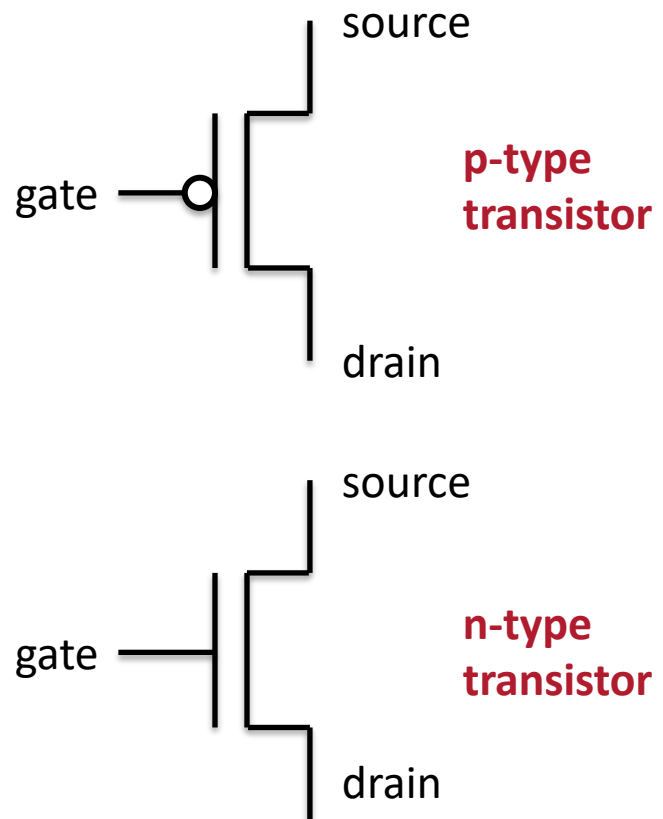
# 🔥 Making a switch out of silicon


- The **transistor**
  - Was invented in 1947 at AT&T's Bell Labs.
- Multiple uses
  - Amplification
  - **Switching**
- Multiple methods of construction
- We are interested in **Integrated Circuits** (ICs), so we want:  
**Complementary Metal–Oxide–Semiconductor (CMOS)** technology.




# n-type and p-type transistors



**n-type transistor**

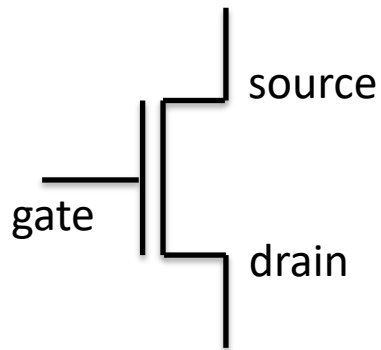


**p-type transistor**

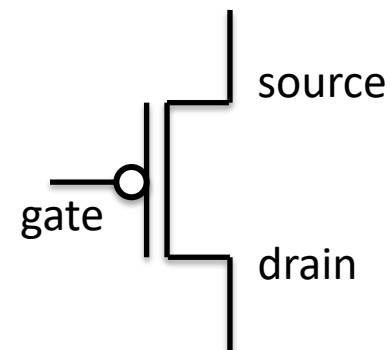


# n-type and p-type transistors



**n-type transistor**

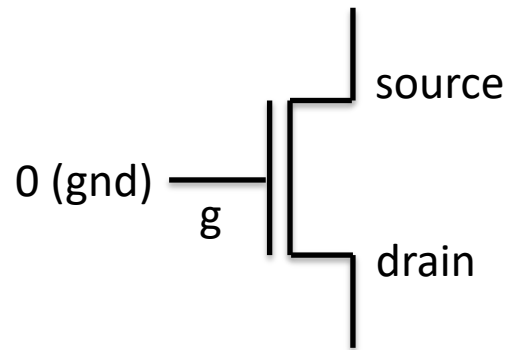

**p-type transistor**

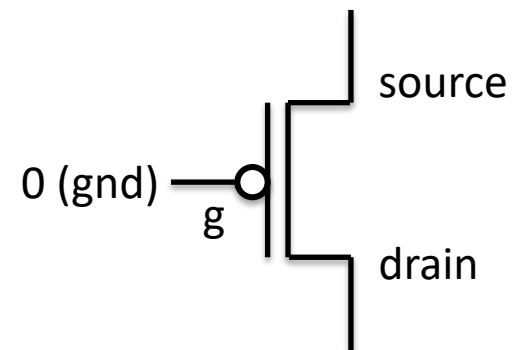





# n-type and p-type transistors



**n-type transistor**

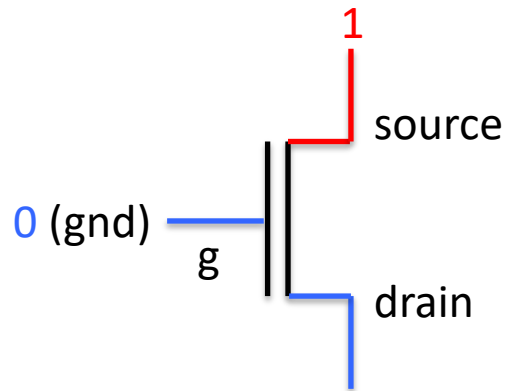

**p-type transistor**


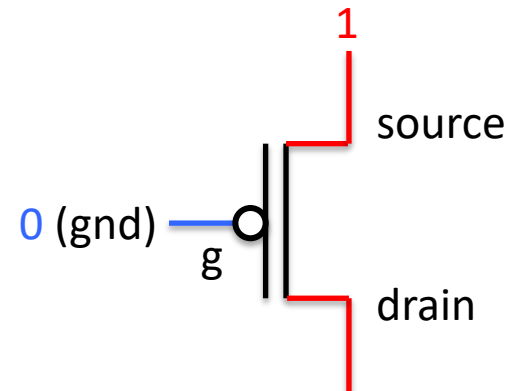


# 🔥 n-type and p-type transistors





**n-type transistor**

**p-type transistor**

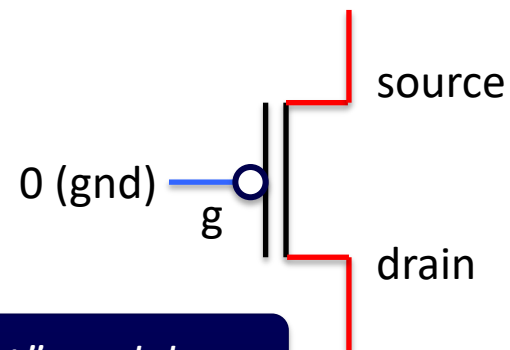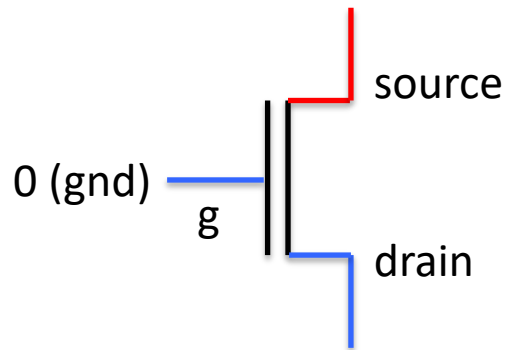

*A simple “thought” model:*

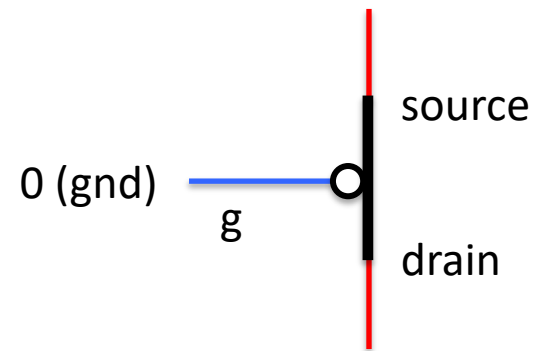
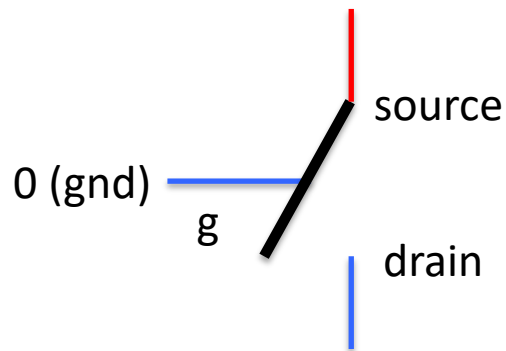


# 🔥 n-type and p-type transistors





**n-type transistor**

**p-type transistor**

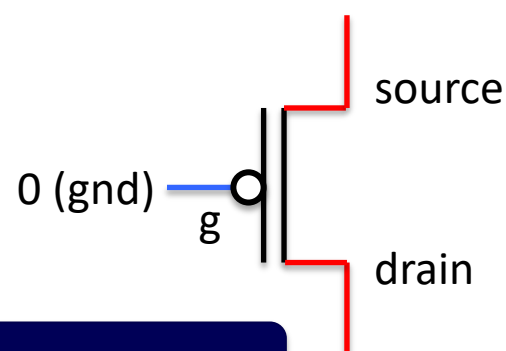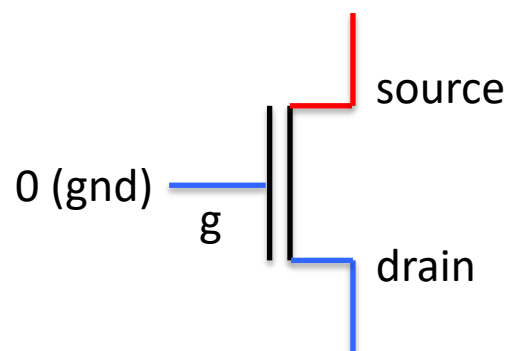


*A simple "thought" model:*

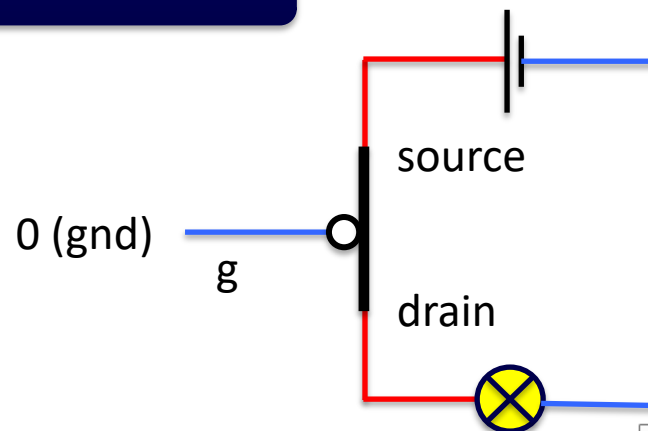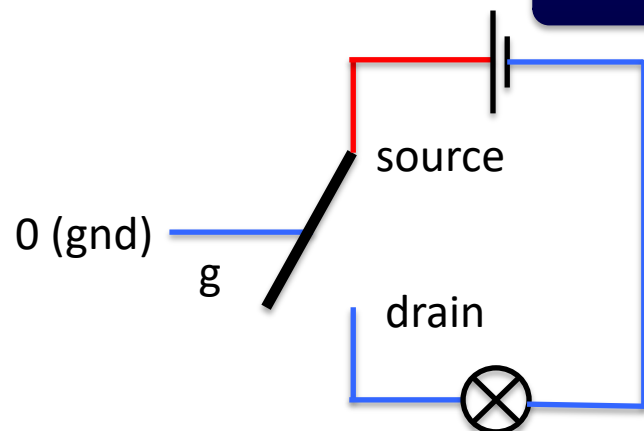


# n-type and p-type transistors



**n-type transistor**

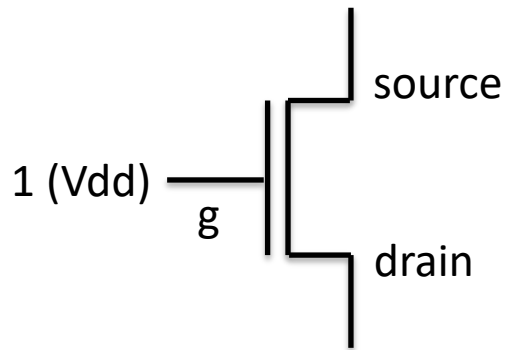


**p-type transistor**

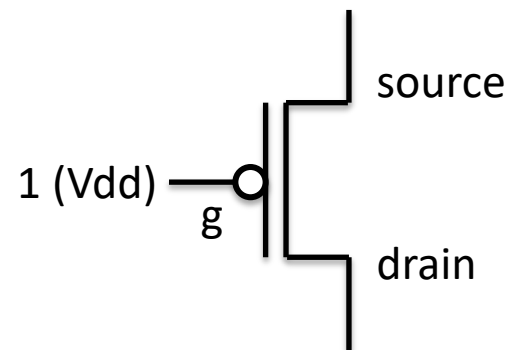


# n-type and p-type transistors



**n-type transistor**

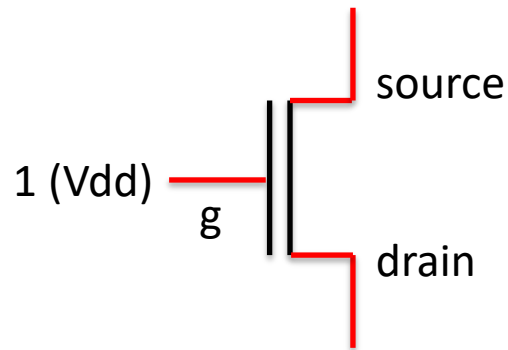

**p-type transistor**


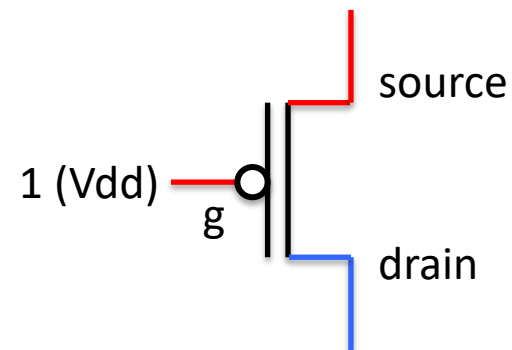


# 🔥 n-type and p-type transistors





**n-type transistor**

**p-type transistor**

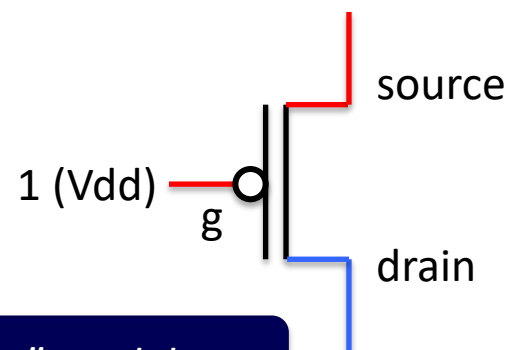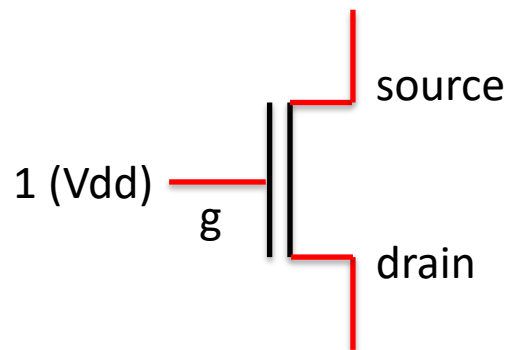

*A simple "thought" model:*

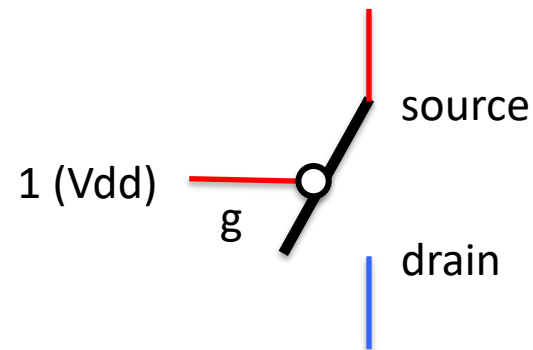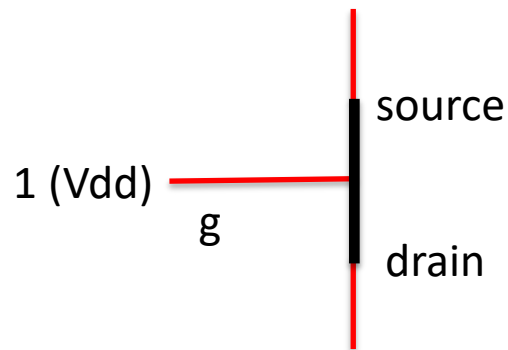





# 🔥 n-type and p-type transistors





**n-type transistor**

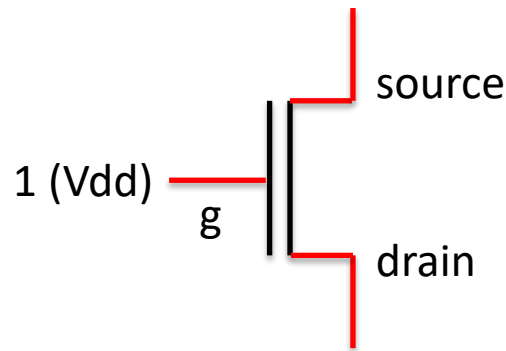

**p-type transistor**

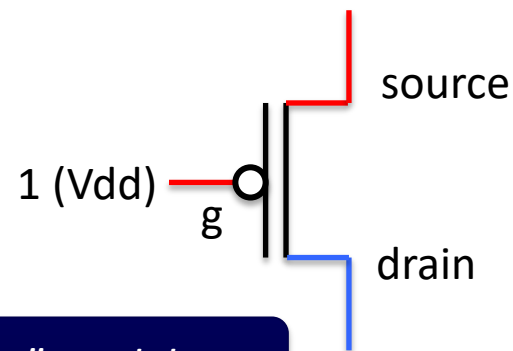

*A simple “thought” model:*

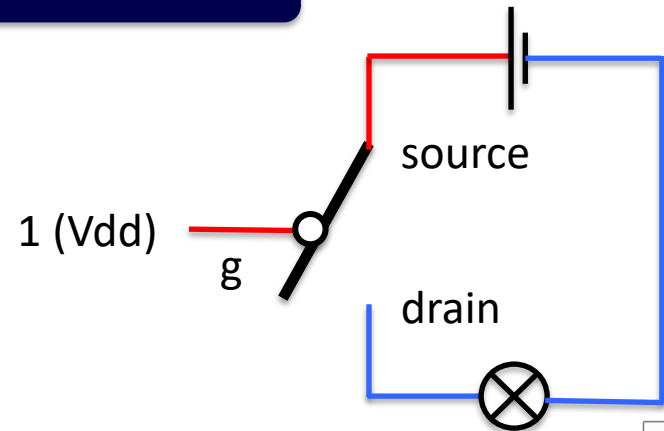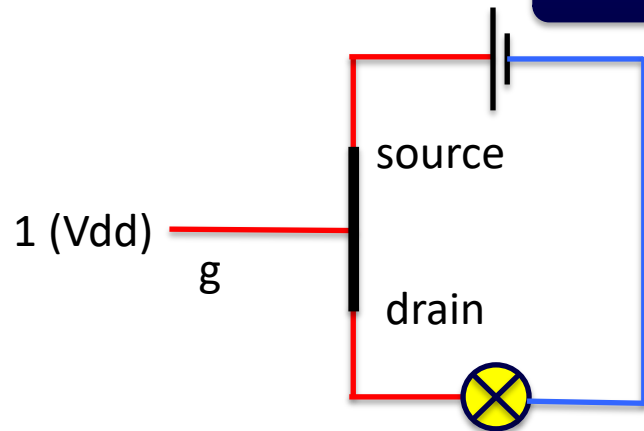


# 🔥 The most basic CMOS circuit

Composition of two **complementary** transistors


- The power supplies for CMOS are called  $V_{dd}$  and  $V_{ss}$ 
  - $V_{dd}$  = drain supply
  - $V_{ss}$  = source supply
    - “0 V” or “ground” voltage

**How does this work?**

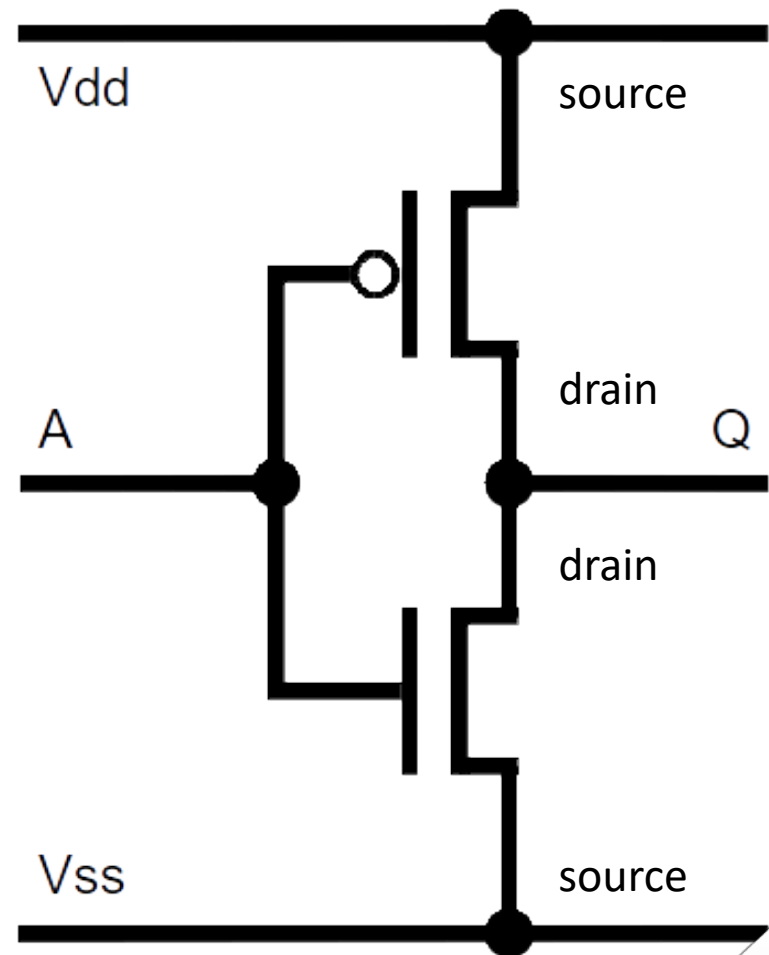

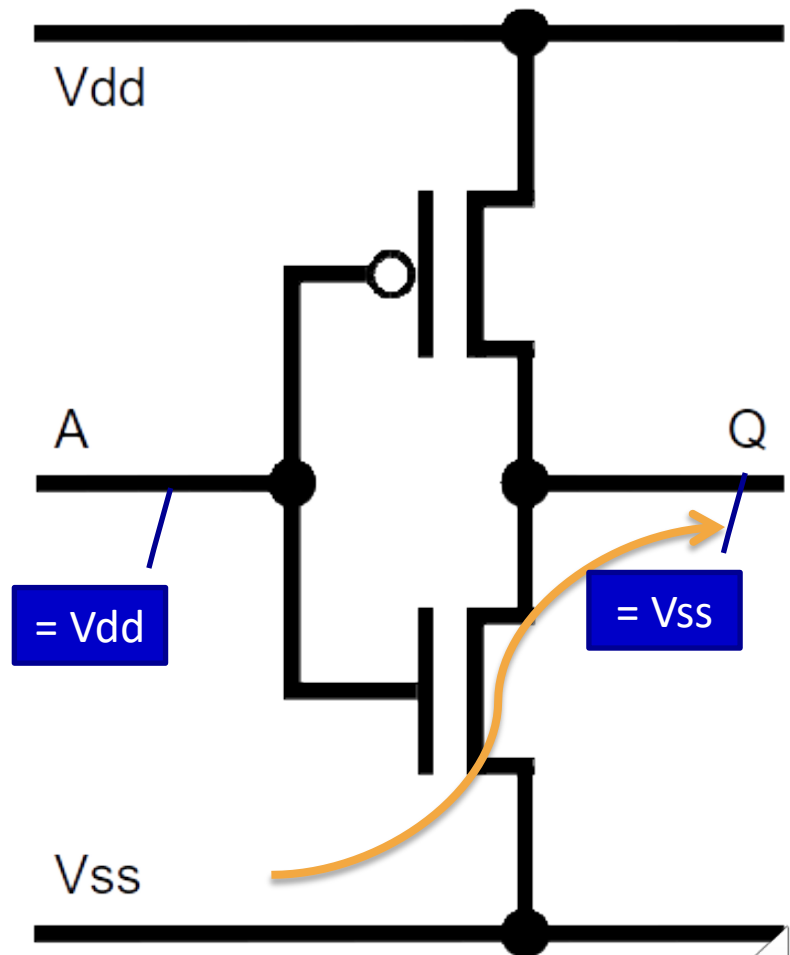
# 🔥 Modes of operation

- $A = V_{dd}$ .
- The top “switch” is **off/open**.
  - PMOS transistor.
- The bottom “switch” is **on/closed**.
  - NMOS transistor
- $Q$  is “connected” to  $V_{ss}$ .




# 🔥 Modes of operation

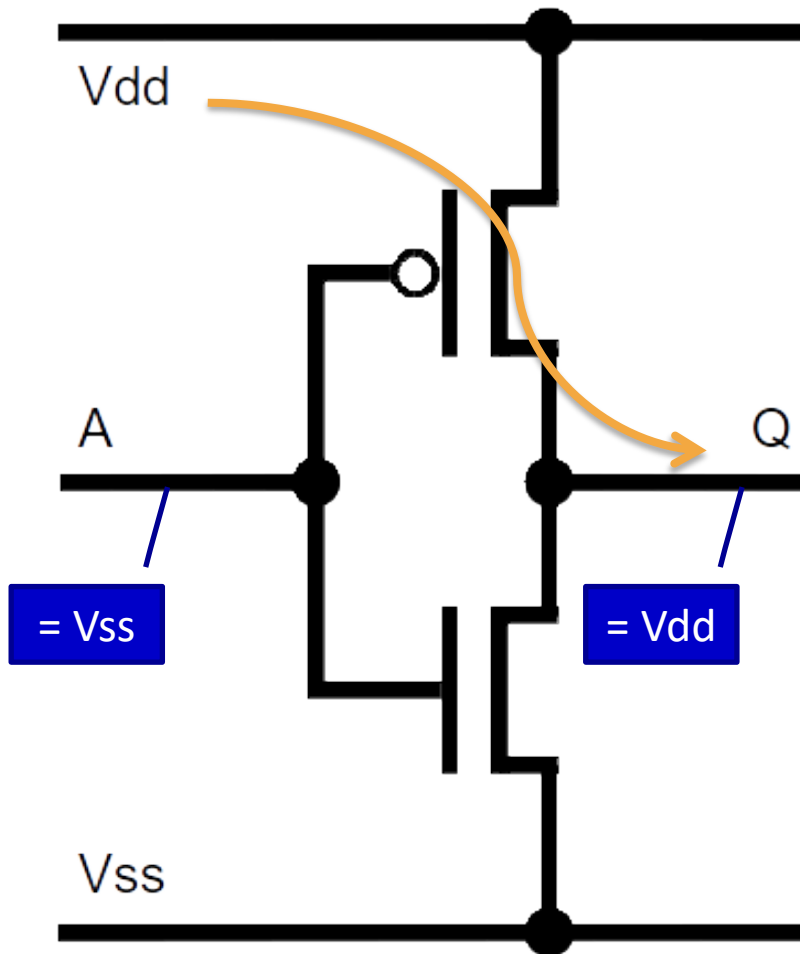

- $A = V_{ss}$ .
- The top “switch” is **on/closed**.
- The bottom “switch” is **off/open**.
- Q is “connected” to Vdd.
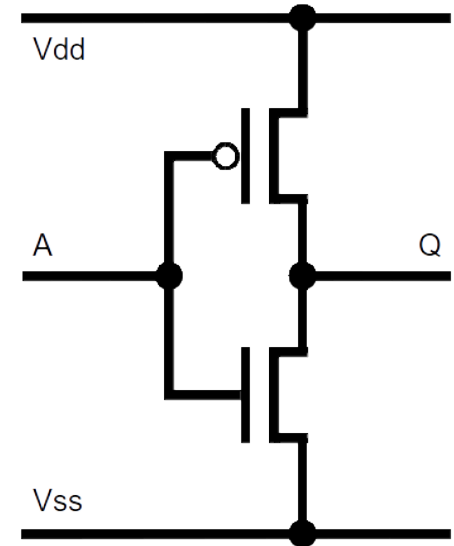
# 🔥 What did we just make?

- The circuit has **four connections**.
- Two are **power-supply** related.
  - Providing Vdd and Vss.
- One is an **input, A**.
- One is an **output, Q**.




## 🔥 Symbolic

## 🔥 Voltage

A	Q	A	Q
Vss	Vdd	0 V	3.3 V
Vdd	Vss	3.3 V	0 V
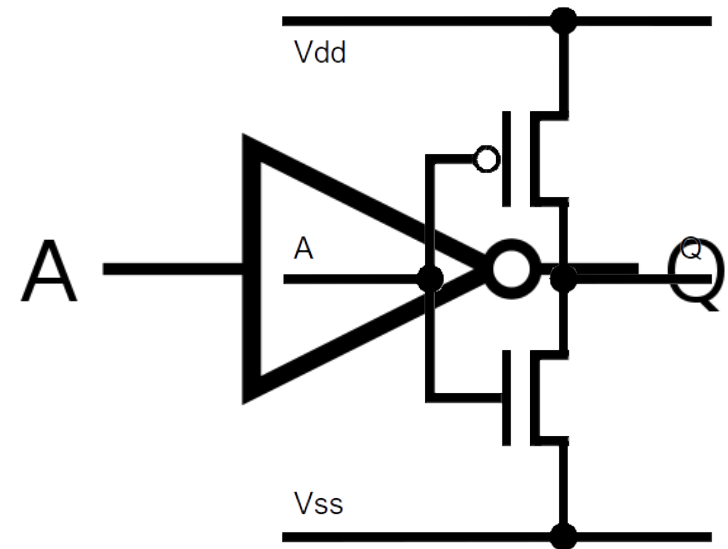
# 🔥 What did we just make?

- The circuit has **four connections**.
- Two are **power-supply** related.
  - Providing Vdd and Vss.
- One is an **input, A**.
- One is an **output, Q**.



## 🔥 Symbolic

## 🔥 Voltage

## 🔥 Binary

A	Q
Vss	Vdd
Vdd	Vss

A	Q
0 V	3.3 V
3.3 V	0 V


A	Q
0	1
1	0




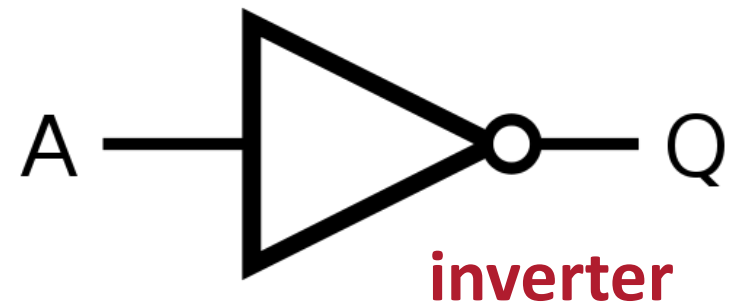
# 🔥 What did we just make?

- The circuit has **four connections**.
- Two are **power-supply** related.
  - Providing Vdd and Vss.
- One is an **input, A**.
- One is an **output, Q**.



## 🔥 Symbolic

A	Q
Vss	Vdd
Vdd	Vss

## 🔥 Voltage

A	Q
0 V	3.3 V
3.3 V	0 V

## 🔥 Binary

A	Q
0	1
1	0




# 🔥 The CMOS inverter

Logisim design of a CMOS inverter for our next lab.

- You can download Logisim from:

<http://sourceforge.net/projects/circuit/>

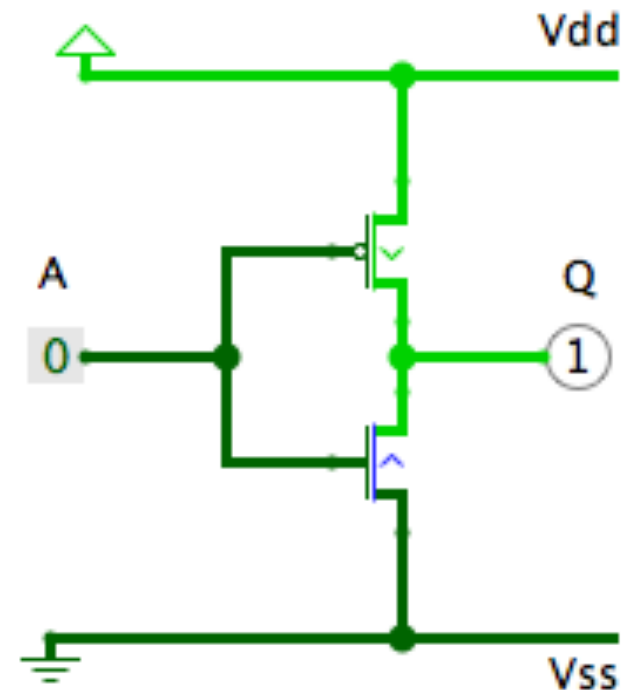- Install Logisim on your own computer and practice outside of lab hours.



NOT




# 🔥 The CMOS inverter

Logisim design of a CMOS inverter for our next lab.

- You can download Logisim from:

<http://sourceforge.net/projects/circuit/>

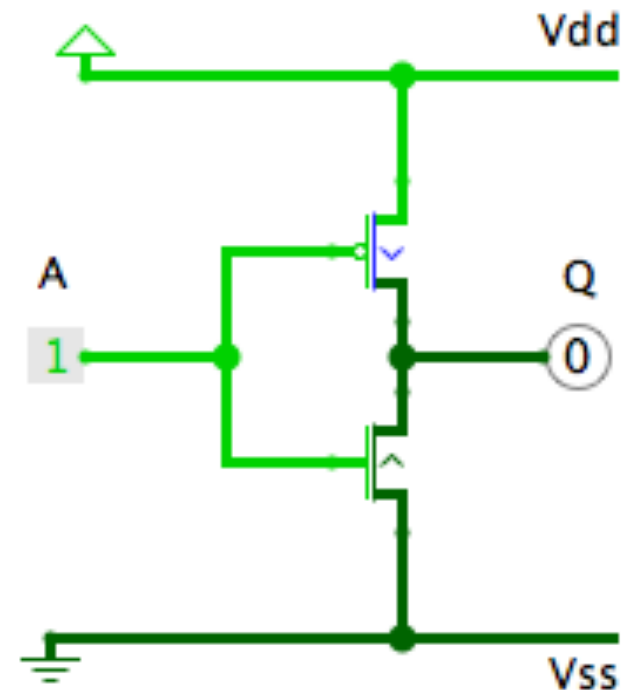
- Install Logisim on your own computer and practice outside of lab hours.



NOT
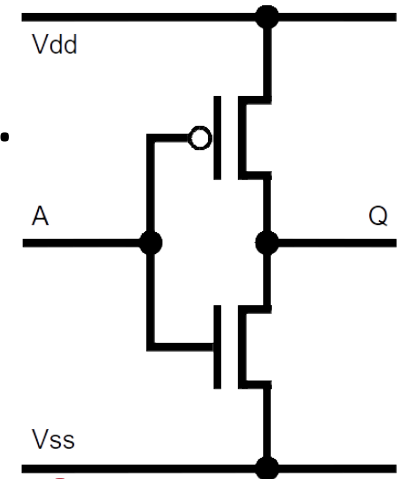
# PMOS + NMOS = CMOS

- PMOS is good for making connections to **Vdd**.
- NMOS is good for making connections to **Vss**.
  - You can't make a reliable switch (or inverter) with just one type.
  - We either get 1/? or ?/0; we want 1/0.
- So we use a **pair**, one PMOS, one NMOS.
- They are **complementary**.



## CMOS

## Complementary Metal Oxide Semiconductor


# Boolean logic in CMOS

- We have a CMOS inverter.
  - Implements “not”
  - In a logic circuit, we call this a **NOT gate**.
- To build a more complex circuit, we need more than just a not gate.

**So ... what (else) can we make?**



# 🔥 So ... what (else) can we make?

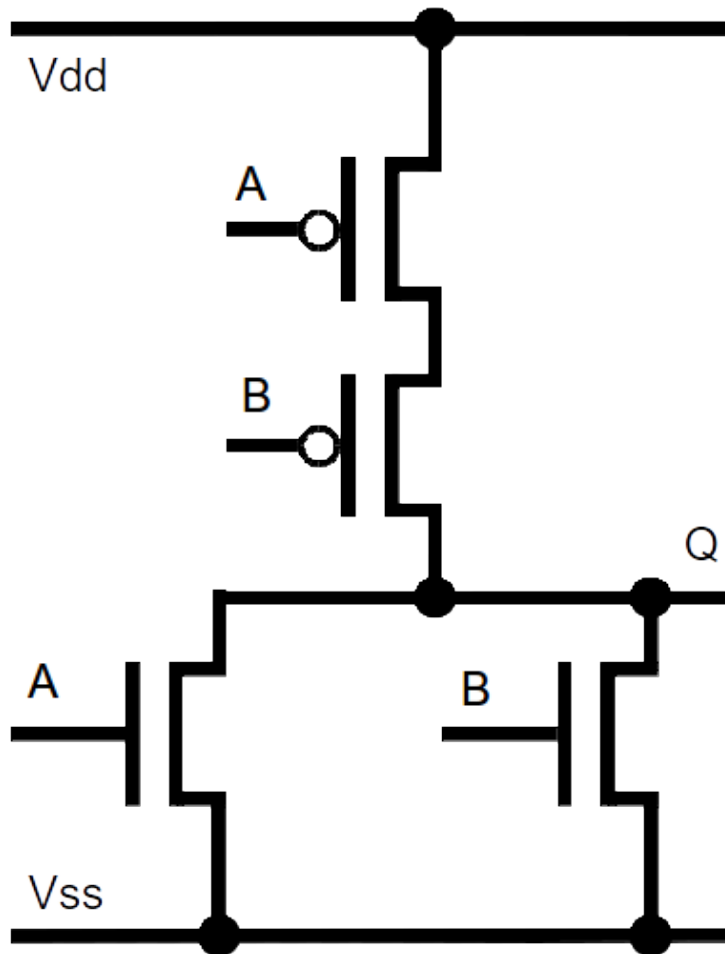


**What is this?**  
**How does it work?**





# 🔥 So ... what (else) can we make?

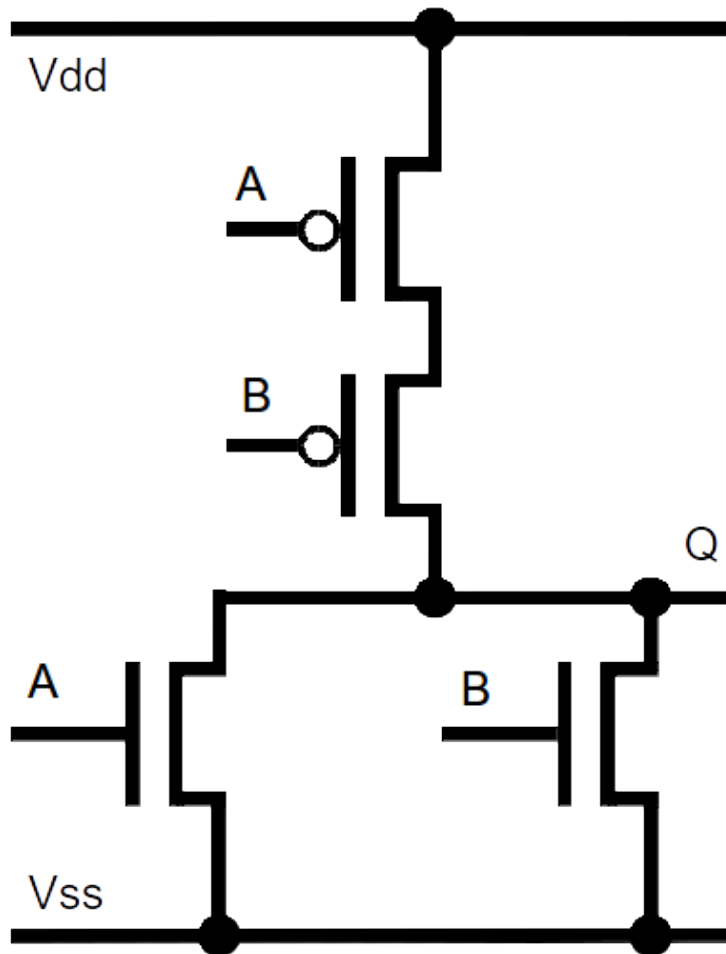


**What is this?**

**How does it work?**

**Please pause to see whether you can work this out. Carry on only when you've tried.**




# 🔥 So ... what (else) can we make?

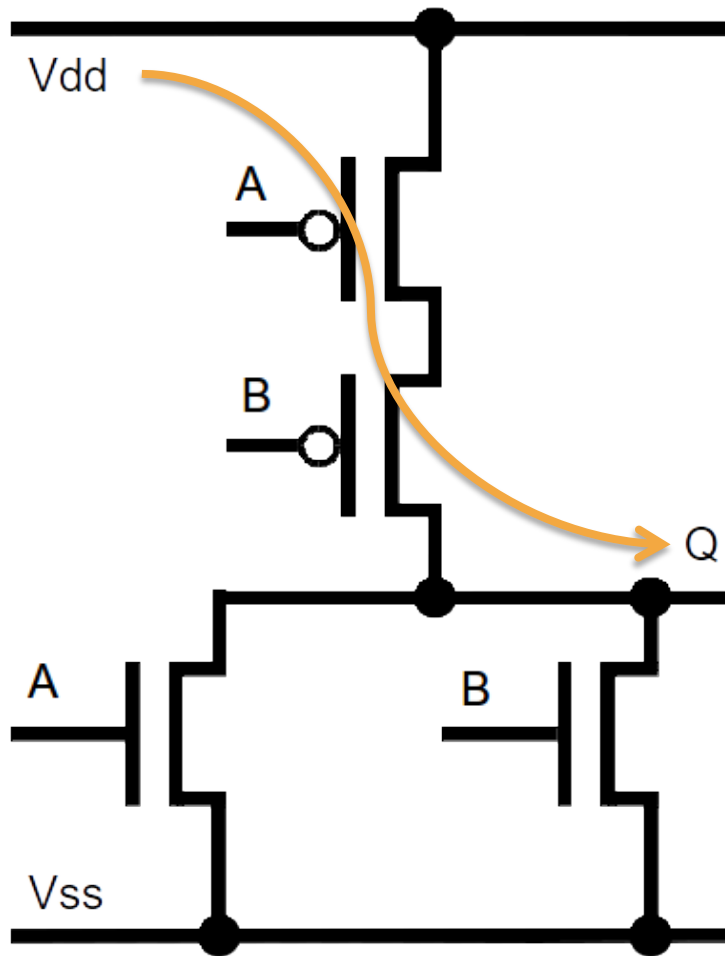

**What is this?**  
**How does it work?**




# 🔥 So ... what (else) can we make?

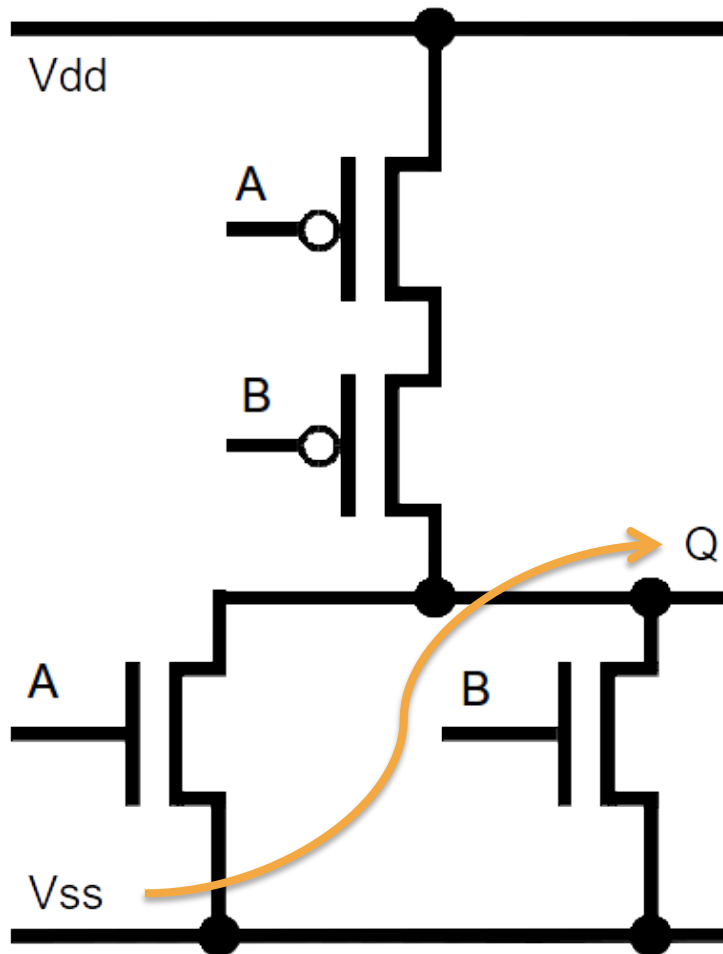


**What is this?**  
**How does it work?**




# NOR (NOT-OR)

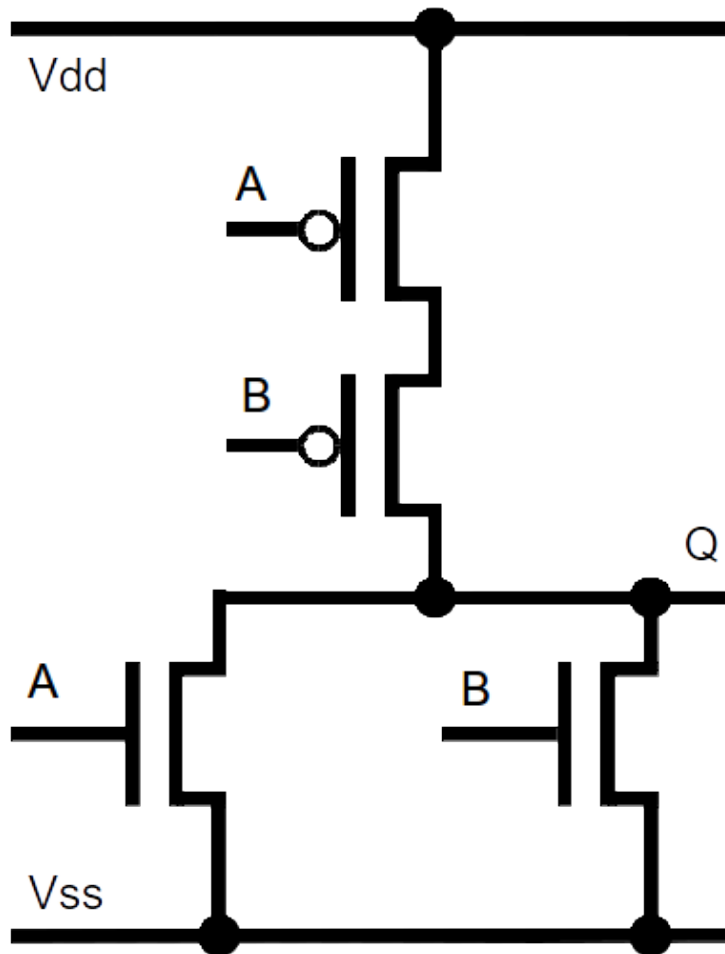


- This is a NOR gate.

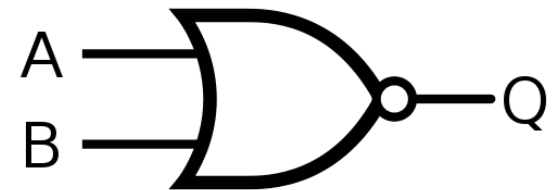

# NOR (NOT-OR)

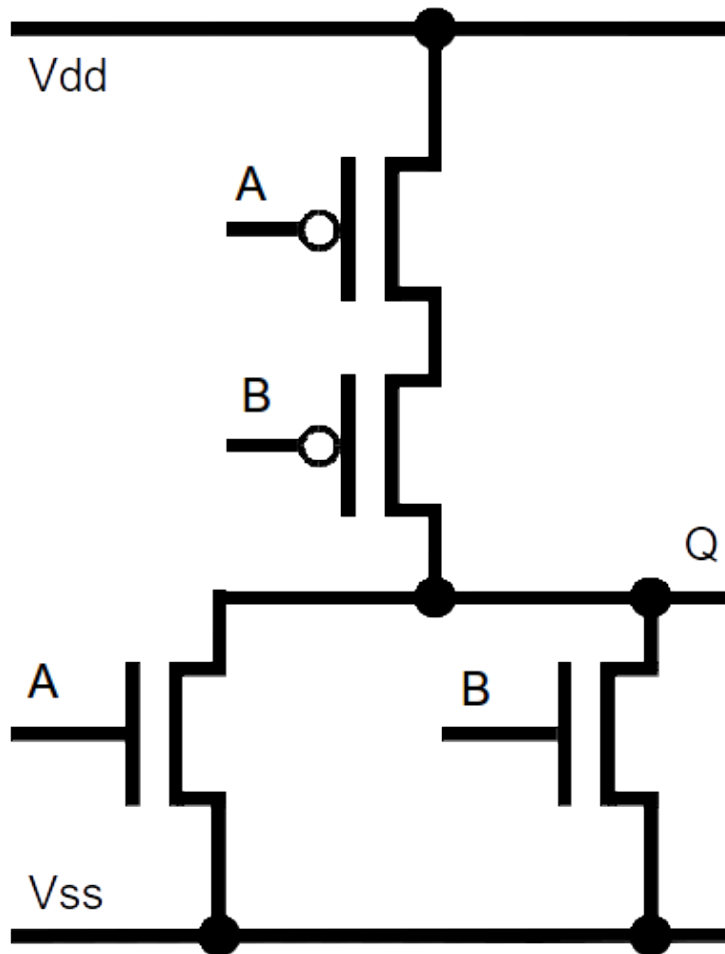


- This is a NOR gate.

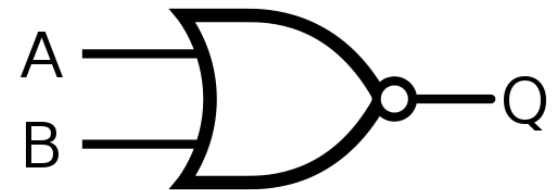


A	B	Q
0	0	
0	1	
1	0	
1	1	



# NOR (NOT-OR)

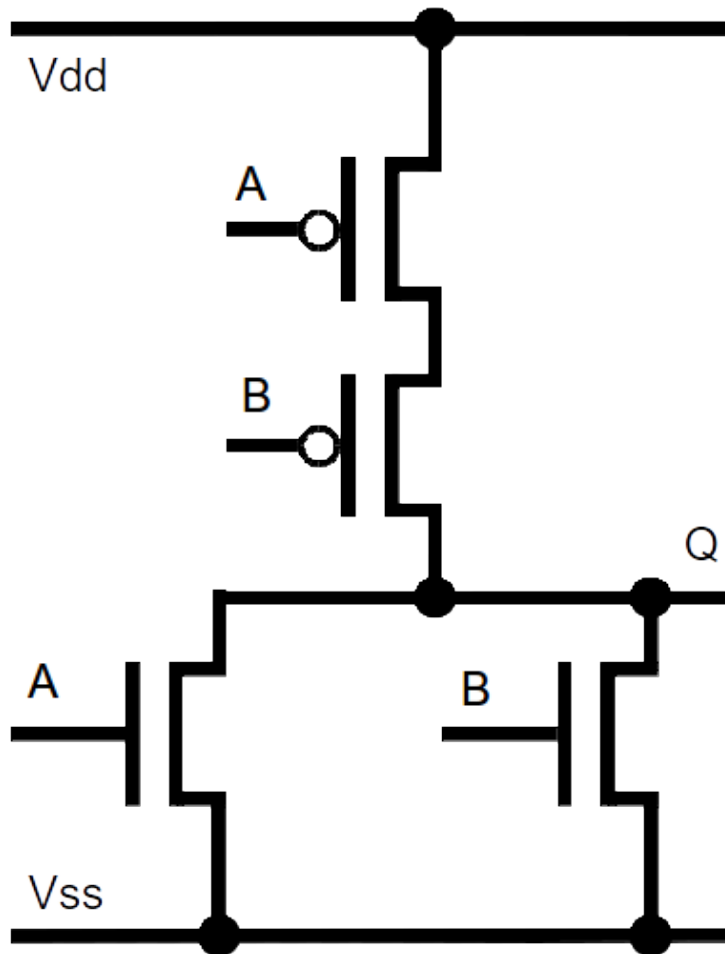


- This is a NOR gate.

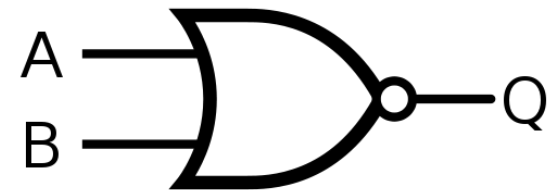

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0




# NAND (NOT-AND)

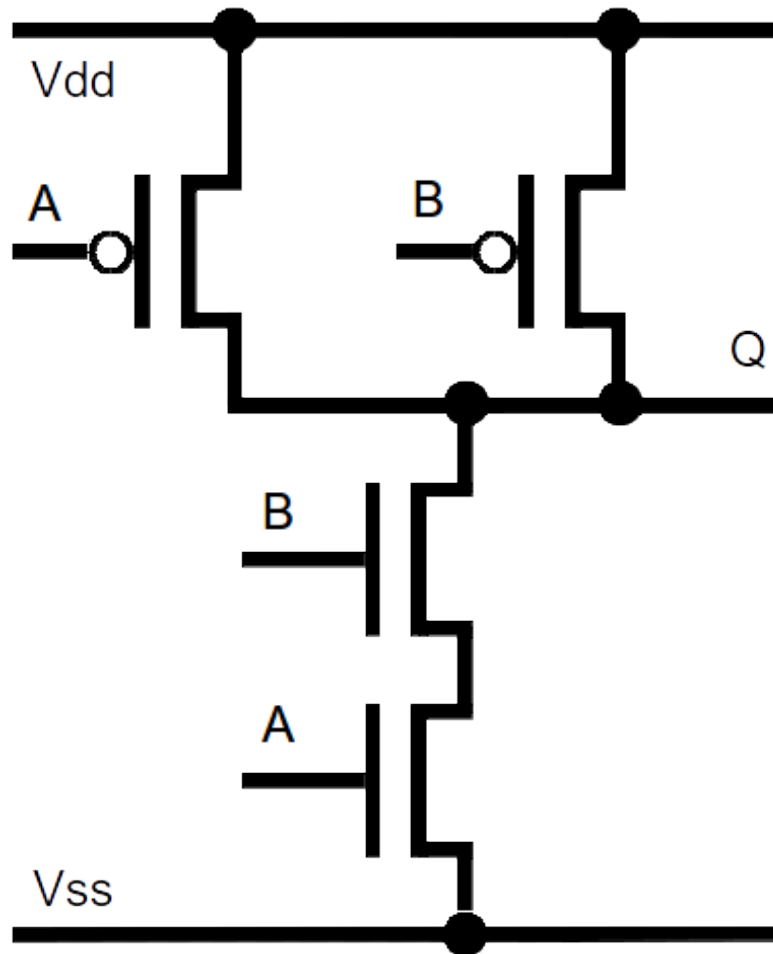

**What is this?**  
**How does it work?**



# 🔥 NAND (NOT-AND)

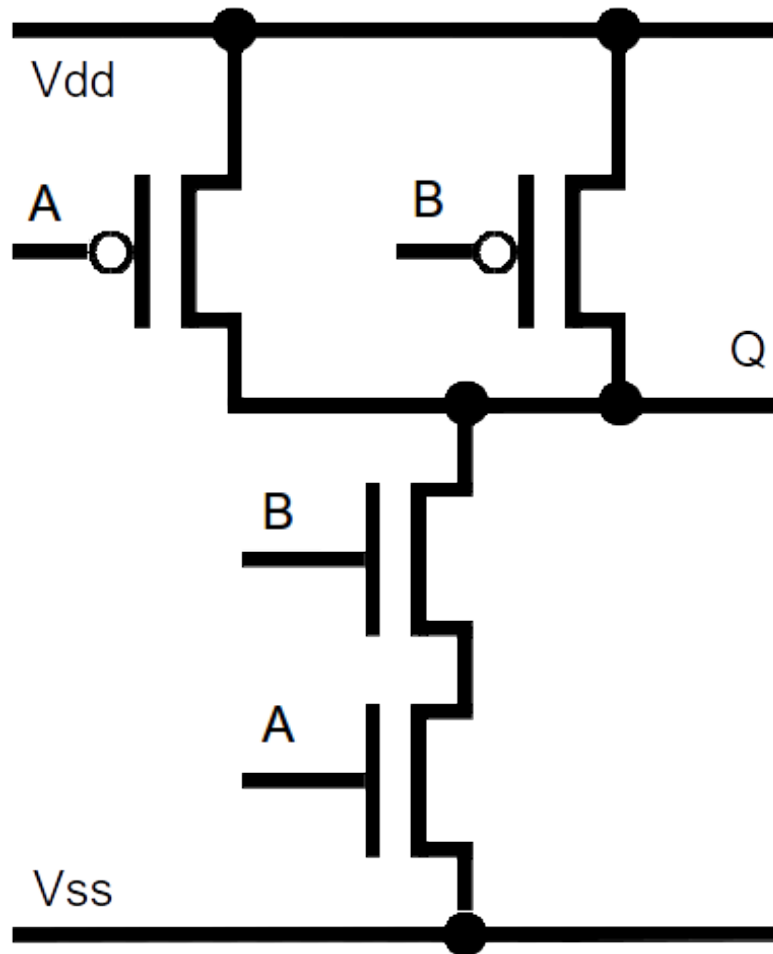


**Can you work out  
under which  
conditions Q is  
connected to Vss?**





# 🔥 NAND (NOT-AND)

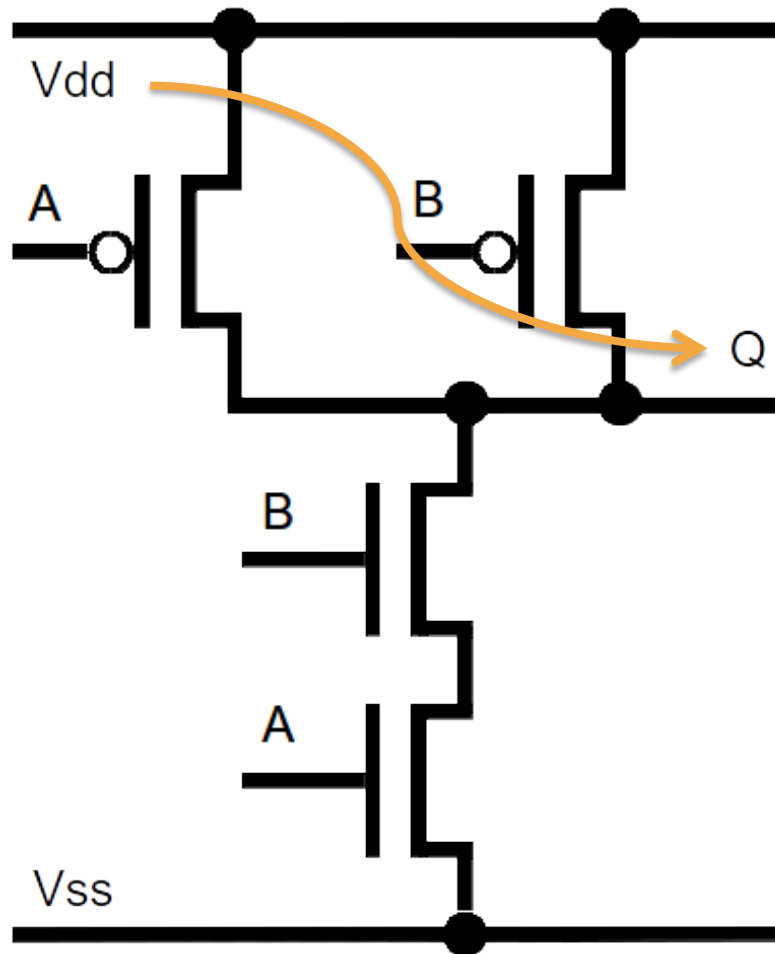


- We could also build a NAND gate.



A	B	Q
0	0	
0	1	
1	0	
1	1	



# 🔥 NAND (NOT-AND)

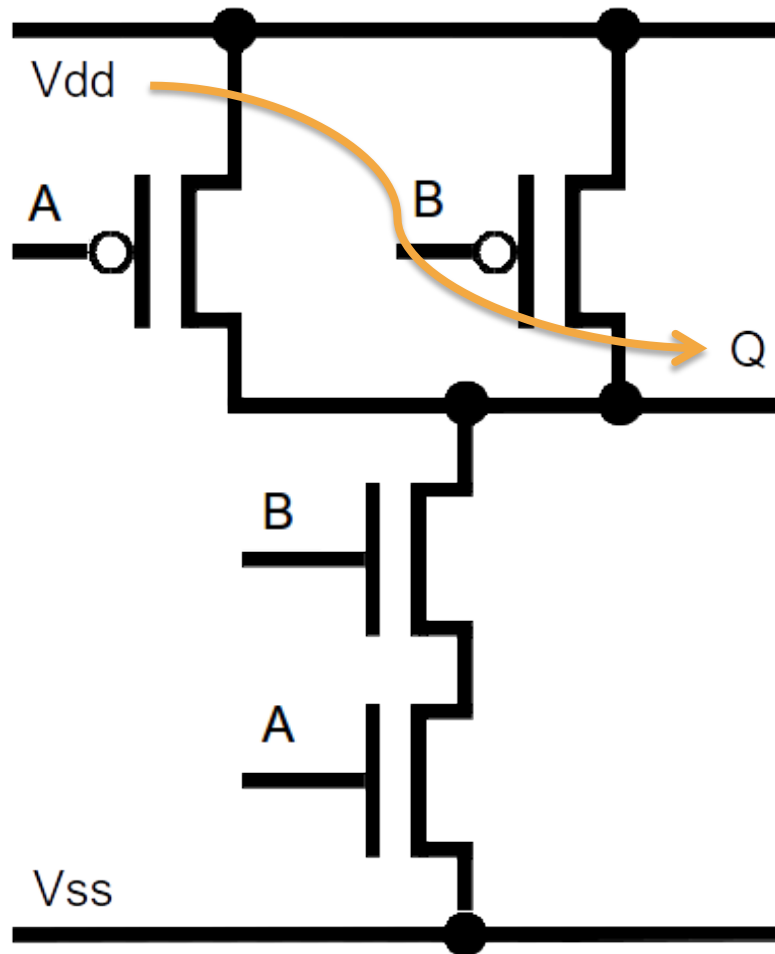


- We could also build a NAND gate.



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	



# 🔥 NAND (NOT-AND)

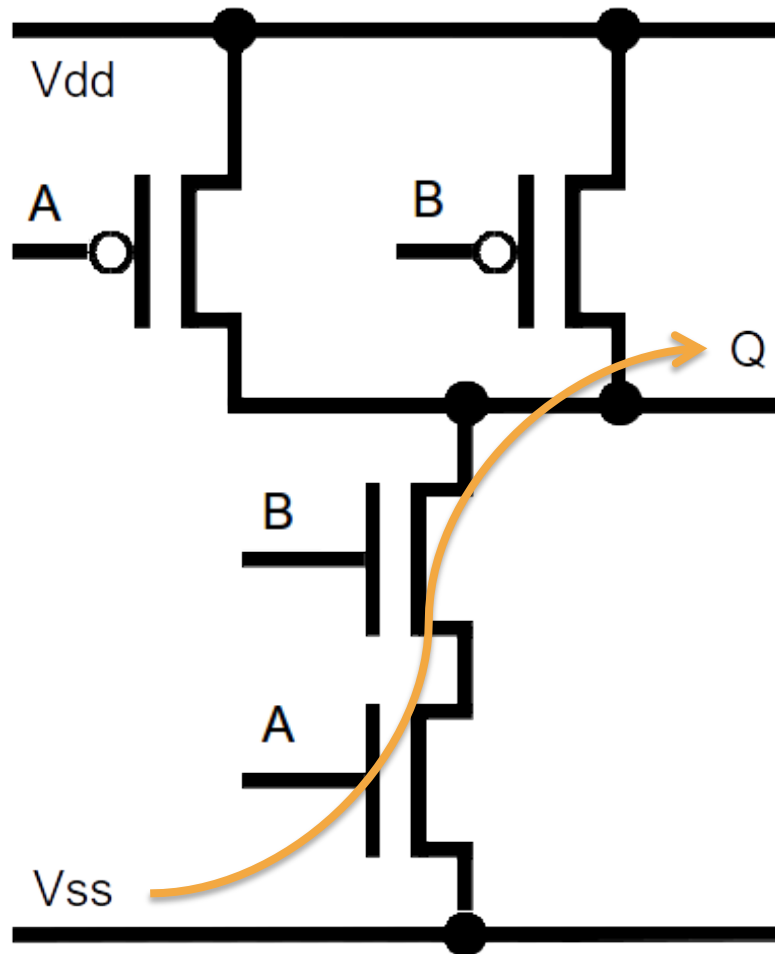


- We could also build a NAND gate.



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	



# 🔥 NAND (NOT-AND)

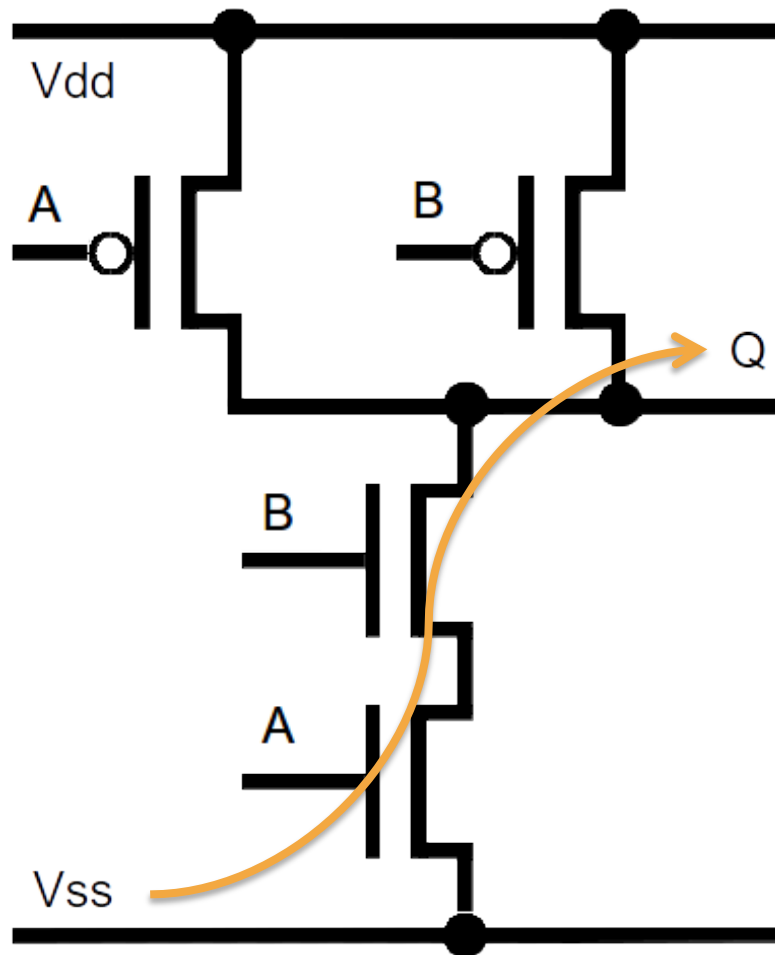


- We could also build a NAND gate.



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0



# 🔥 NAND (NOT-AND)

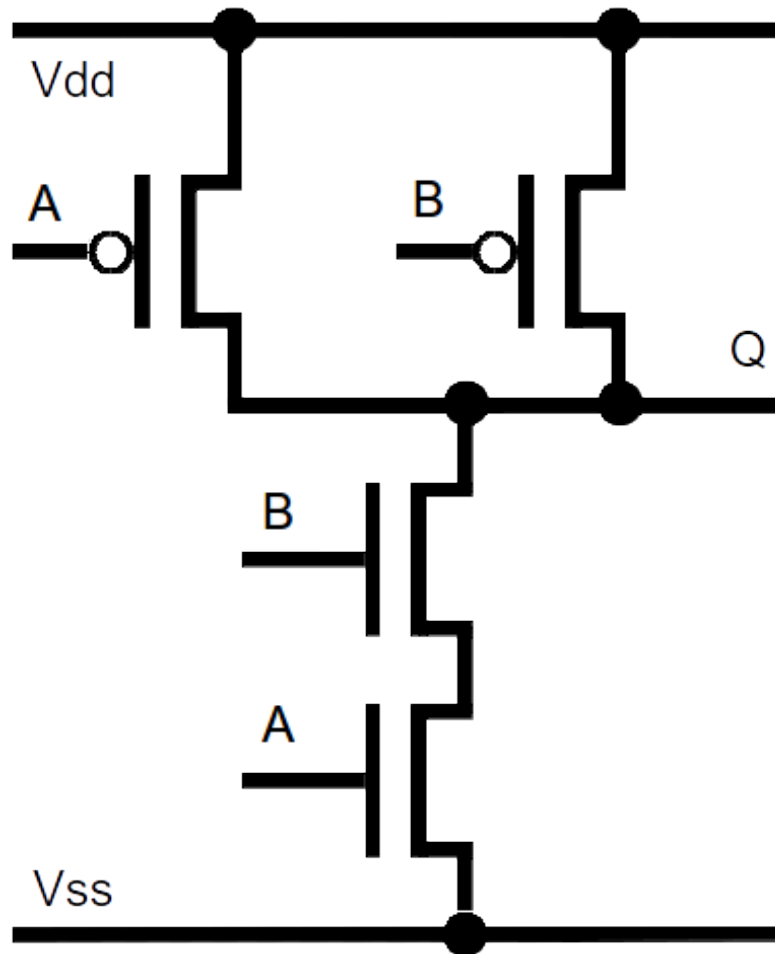


- We could also build a NAND gate.




A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0



# NOR and NAND in Logisim

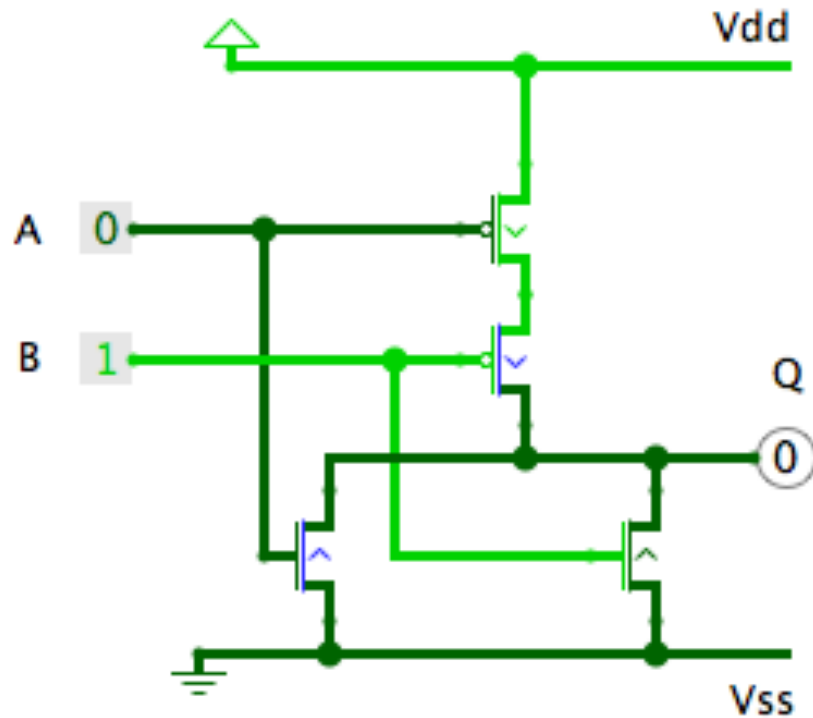

NOR

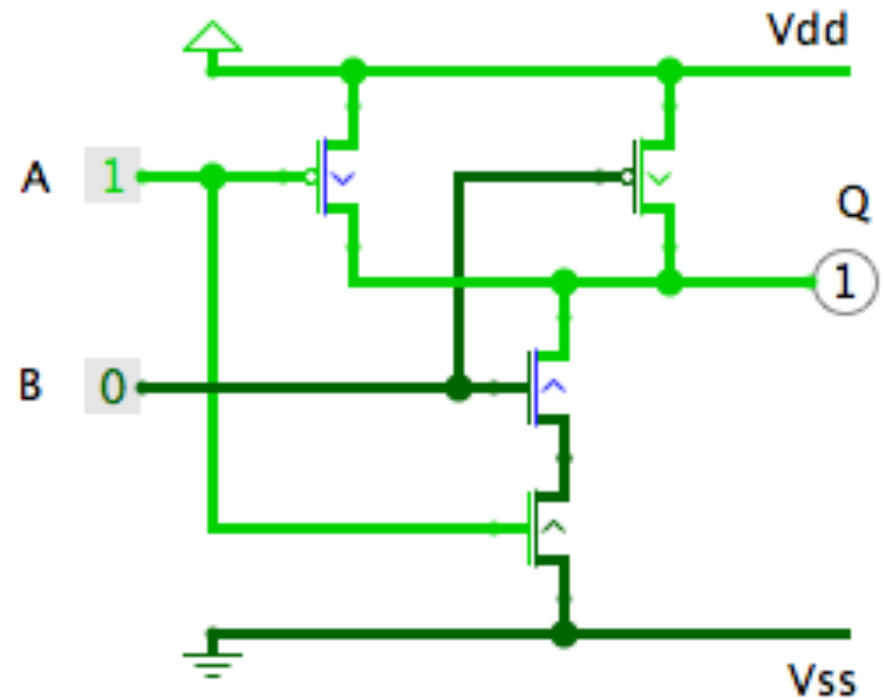

NAND

# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **NOT**  A —  Q

## 🔥 Diagram



## 🔥 Boolean algebra

$$Q = \neg(A \wedge A)$$

- Idempotence axiom

## 🔥 Truth table

A	Q
0	1
1	0

# Axioms in Boolean algebra

- Some rules help us avoid evaluating parts, because we can know the answer regardless of the values of the variables.

Rule	Axioms
Identity	$x \wedge 1 \equiv x$
Null	$x \wedge 0 \equiv 0$
Idempotence	$x \wedge x \equiv x$
Inverse	$x \wedge \neg x \equiv 0$

From Lecture 2  
Boolean Algebra

- Duality:** Swap 0s and 1s, conjunction and disjunction. Equivalence property is preserved.



# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **NOT**  A —  Q

## 🔥 Diagram



## 🔥 Boolean algebra

$$Q = \neg(A \wedge A)$$

- Idempotence axiom

$$x \wedge x \equiv x$$

$$\neg(\underline{A \wedge A}) \equiv \neg(\underline{A}) \equiv \neg \underline{A}$$

## 🔥 Truth table

A	Q
0	1
1	0



# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **NOT**  A —  Q

## 🔥 Diagram



## 🔥 Boolean algebra

$$Q = \neg(A \wedge A) = \neg A$$

- Idempotence axiom

$$x \wedge x \equiv x$$

$$\neg(\underline{A \wedge A}) \equiv \neg(\underline{A}) \equiv \neg \underline{A}$$

## 🔥 Truth table

A	Q
0	1
1	0




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

## 🔥 Diagram

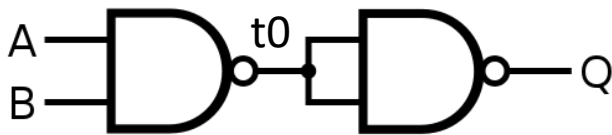

$$t0 = \neg( A \wedge B )$$

## 🔥 Algebra

$$Q = \neg(t0)$$

## 🔥 Truth table

A	B	t0	Q
0	0		
0	1		
1	0		
1	1		




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

## 🔥 Diagram

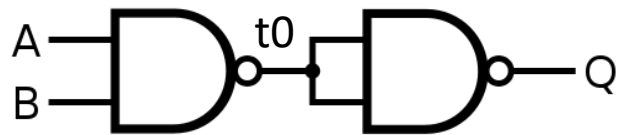

$$t0 = \neg( A \wedge B )$$

## 🔥 Algebra

$$\begin{aligned} Q &= \neg( \neg( A \wedge B ) ) \\ &= A \wedge B \end{aligned}$$

- Double negation axiom  
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

## 🔥 Truth table

A	B	t0	Q
0	0		
0	1		
1	0		
1	1		




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

## 🔥 Diagram

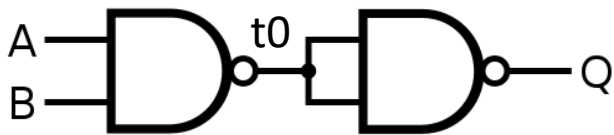

## 🔥 Algebra

$$Q = \neg(\neg(A \wedge B)) \\ = A \wedge B$$

- Double negation axiom  
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

## 🔥 Truth table

A	B	t0	Q
0	0	1	
0	1	1	
1	0	1	
1	1	0	




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

## 🔥 Diagram

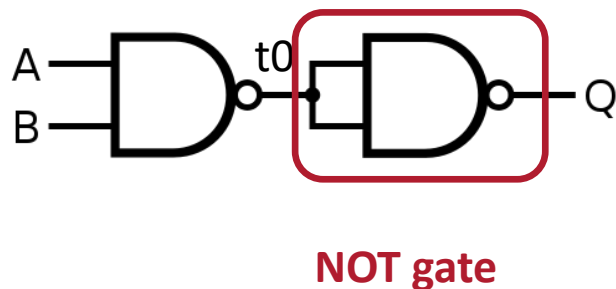

## 🔥 Algebra

$$Q = \neg(\neg(A \wedge B))$$
$$= A \wedge B$$

- Double negation axiom  
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

## 🔥 Truth table

A	B	t0	Q
0	0	1	
0	1	1	
1	0	1	
1	1	0	




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

## 🔥 Diagram

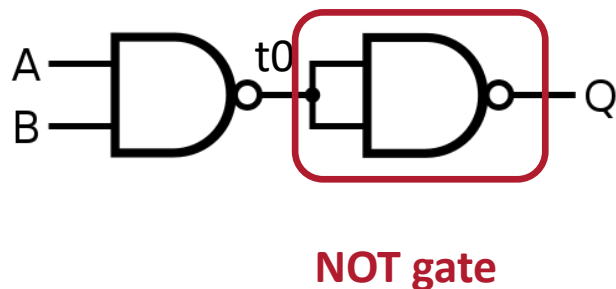

## 🔥 Algebra

$$Q = \neg( \neg( A \wedge B ) )$$
$$= A \wedge B$$

- Double negation axiom  
 $\neg(\neg X) \equiv \neg\neg X \equiv X$

## 🔥 Truth table

A	B	t0	Q
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

## 🔥 Diagram

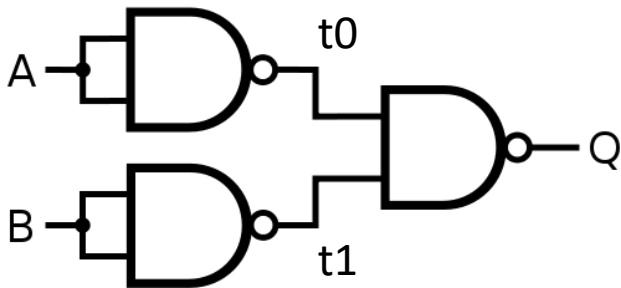

## 🔥 Algebra

$$Q =$$

## 🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			






# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

## 🔥 Diagram

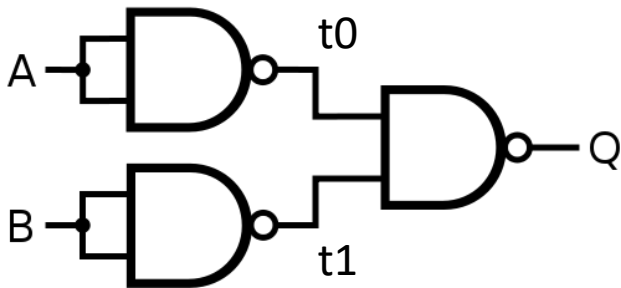

## 🔥 Algebra

$$Q = \neg(t0 \wedge t1)$$

$$t0 = \neg(A \wedge A)$$

$$t1 = \neg(B \wedge B)$$

## 🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

## 🔥 Diagram

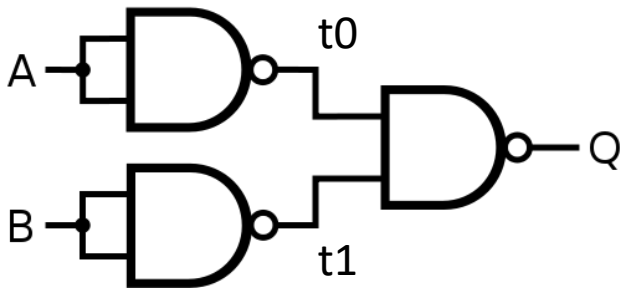

## 🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$

## 🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			




# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

## 🔥 Diagram

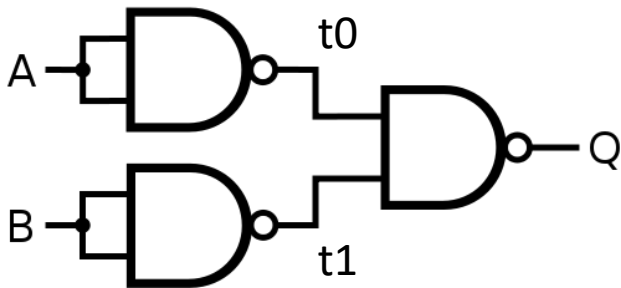

## 🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$

- Idempotence, de Morgan and double negation

## 🔥 Truth table

A	B	t0	t1	Q
0	0			
0	1			
1	0			
1	1			




# 🔥 Why NAND?



- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

## 🔥 Diagram

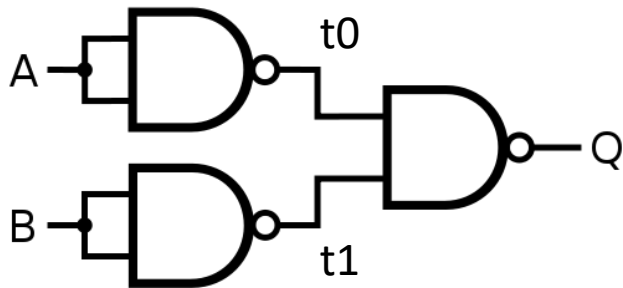

## 🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$

- Idempotence, de Morgan and double negation

## 🔥 Truth table

A	B	t0	t1	Q
0	0	1	1	
0	1	1	0	
1	0	0	1	
1	1	0	0	




# 🔥 Why NAND?



- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR** 

## 🔥 Diagram

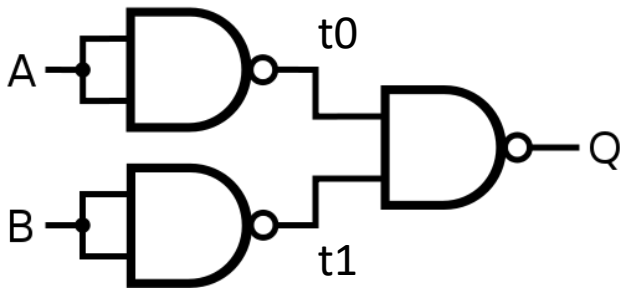

## 🔥 Algebra

$$\begin{aligned} Q &= \neg(\neg(A \wedge A) \wedge \neg(B \wedge B)) \\ &= \neg(\neg A \wedge \neg B) \\ &= \neg(\neg(A \vee B)) \\ &= A \vee B \end{aligned}$$


- Idempotence, de Morgan and double negation

## 🔥 Truth table

A	B	t0	t1	Q
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1




# 🔥 Why NAND?

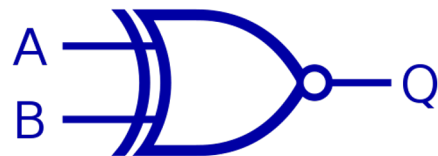

- NAND is an excellent **building block** for other Boolean logic.
- **NAND is functionally complete.**
  - All gates can be expressed with NAND gates arranged in various ways.
- **NOT, AND, OR** as previously shown.
- As well as **NOR**, **XOR**, **XNOR**.
  - **NOR** is also functionally complete.
  - **NOR** structure is slower than NAND.

# 🔥 Voltages and logic levels

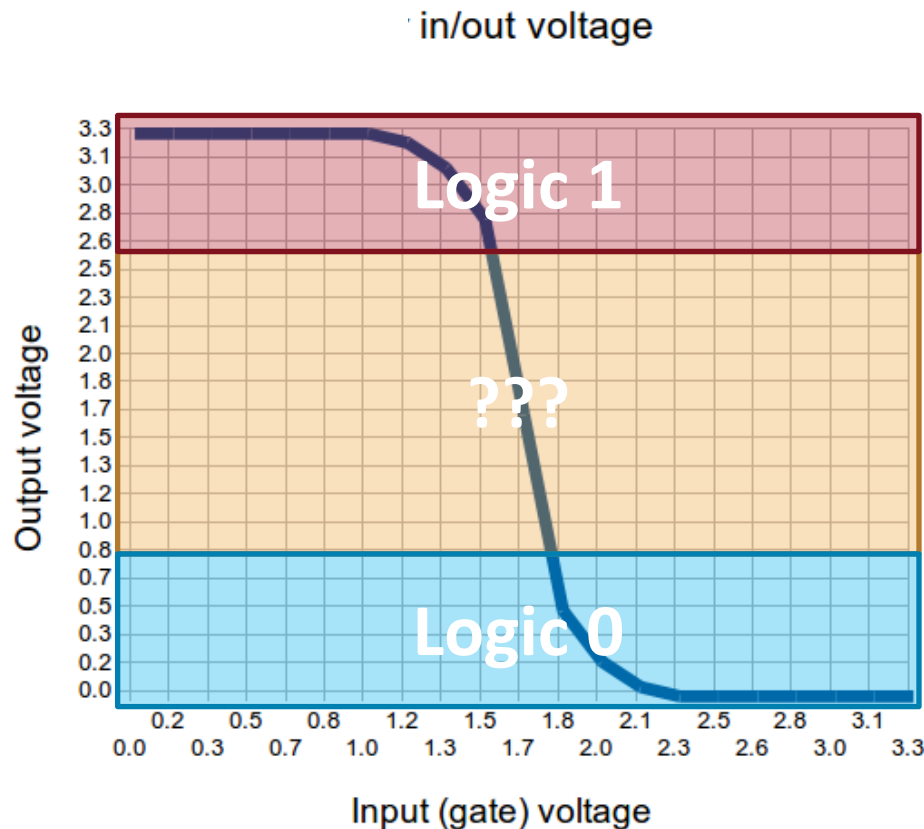

- Simplified view so far.
- **Ideal** would be a **right-angled** response.
- Steepness and position of curve depend on transistor **properties**.
- There is also a **delay** between a change in input producing a change in output.
- This delay accounts for the **physical signal propagation time** in silicon.



# COMSM1302 NAND Lab 1-3




- NAND boards have either been sent to you or are ready for you to collect.
- The NAND boards are for you to work on your lab sheets during scheduled lab hours or on your own.
- **Please be careful with the NAND boards. They have sharp edges and are sensitive electronic devices.**




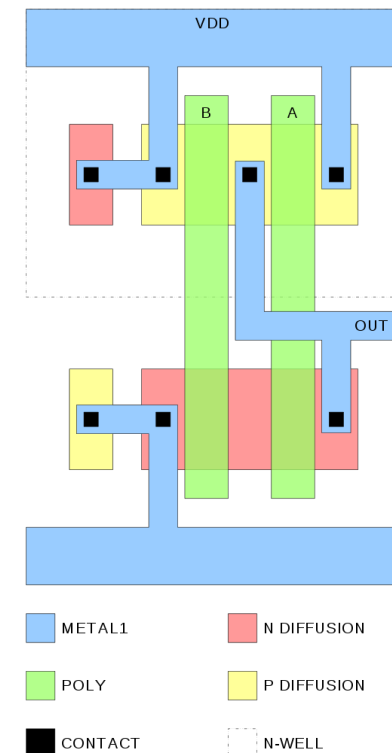
# Summary

- Switches
    - Mechanical
    - Thermionic
    - Silicon
  - Transistors
  - CMOS
    - Inverter
    - NAND (functionally complete)
    - Making other gates from NAND
  - More about how chips are made:
    - <https://www.youtube.com/watch?v=qm67wbB5Gml>
    - <https://www.youtube.com/watch?v=4FLBtQC0F0c>
    - <https://www.youtube.com/watch?v=i8kxymmjd0M>
- and this is also quite cool:
- <https://www.youtube.com/watch?v=Y33cf-lcq-g>



The physical layout of a NAND circuit. [Source: By Jamesm76 at English Wikipedia -

Transferred from en.wikipedia to Commons., Public Domain,  
<https://commons.wikimedia.org/w/index.php?curid=294462>]



# In this lecture

## Foundations

- Data representation, logic, Boolean algebra.

## Building blocks

- **Transistors, transistor based logic**, simple devices, storage.

## Modules

- Memory, simple controllers, FSMs, processors and execution.

## Programming

- Machine code, assembly, high-level languages, compilers.

## Wrap-up

- Operating systems, energy aware computing.



# In the next lecture

## Foundations

- Data representation, logic, Boolean algebra.

## Building blocks

- Transistors, transistor based logic, **simple devices**, storage.

## Modules

- Memory, simple controllers, FSMs, processors and execution.

## Programming

- Machine code, assembly, high-level languages, compilers.

## Wrap-up

- Operating systems, energy aware computing.



